




HACETTEPE UNIVERSITY
ELECTRICAL AND ELECTRONICS ENGINEERING
ELE227 FUNDAMENTALS OF DIGITAL SYSTEMS

PRELIMINARY WORK 5

EGEMEN CAN AYDUĞAN - 21728036

1.A) Universal Shift Register

Circuit Diagram

 

VHDL Implementation:

```

entity UniversalShiftRegister is
    Port ( I : in  STD_LOGIC_VECTOR (3
downto 0);
          S : in  STD_LOGIC_VECTOR (1
downto 0);
          MSB : in  STD_LOGIC;
          LSB : in  STD_LOGIC;
          Clock : in  STD_LOGIC;
          Reset : in  STD_LOGIC;
          O : out  STD_LOGIC_VECTOR (3
downto 0));
end UniversalShiftRegister;

architecture Behavioral of
UniversalShiftRegister is

component TFlipFlop
    Port ( T : in  STD_LOGIC;
          Reset : in  STD_LOGIC;
          Clock : in  STD_LOGIC;
          Q : out  STD_LOGIC;
          Qn : out  STD_LOGIC);
end component;

component MUX
    Port ( I3 : in  STD_LOGIC;
          I2 : in  STD_LOGIC;
          I1 : in  STD_LOGIC;
          I0 : in  STD_LOGIC;
          S : in  STD_LOGIC_VECTOR (1
downto 0);
          O : out  STD_LOGIC);
end component;

    signal A : STD_LOGIC_VECTOR (3 downto 0);
    signal L : STD_LOGIC_VECTOR (3 downto 0);
    signal T : STD_LOGIC_VECTOR (3 downto 0);

begin
    M3 : MUX port
    map(I(3),A(2),MSB,A(3),S,L(3));
    M2 : MUX port
    map(I(2),A(1),A(3),A(2),S,L(2));
    M1 : MUX port
    map(I(1),A(0),A(2),A(1),S,L(1));
    M0 : MUX port
    map(I(0),LSB,A(1),A(0),S,L(0));

    T(3) <= L(3) xor A(3);
    T(2) <= L(2) xor A(2);
    T(1) <= L(1) xor A(1);
    T(0) <= L(0) xor A(0);


    FF3 : TFlipFlop port
    map(T(3),Reset,Clock,A(3));
    FF2 : TFlipFlop port
    map(T(2),Reset,Clock,A(2));
    FF1 : TFlipFlop port
    map(T(1),Reset,Clock,A(1));
    FF0 : TFlipFlop port
    map(T(0),Reset,Clock,A(0));

    O(3) <= A(3);
    O(2) <= A(2);
    O(1) <= A(1);
    O(0) <= A(0);

end Behavioral;

```

RTL Schematic:

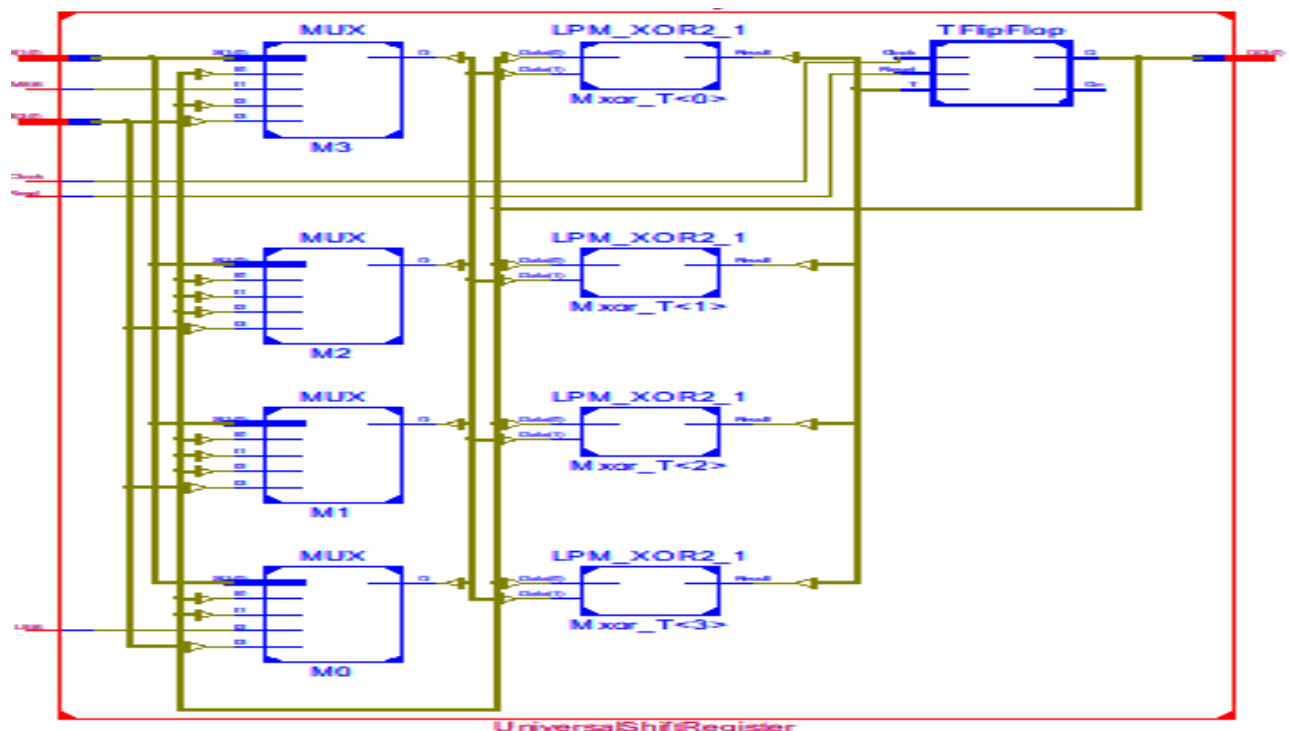

Test Bench Input:

```

signal I : std_logic_vector(3 downto 0)
:= (others => '0');
signal S : std_logic_vector(1 downto
0) := (others => '0');
signal MSB : std_logic := '0';
signal LSB : std_logic := '0';
signal Clock : std_logic := '0';
signal Reset : std_logic := '1';

signal O : std_logic_vector(3 downto
0);

constant Clock_period : time := 100
ns;

Clock_process : process
begin
    Clock <= '0';
    wait for Clock_period/2;
    Clock <= '1';
    wait for Clock_period/2;
end process;

```


```

stim_proc: process
begin
    Reset <= '1';
    wait for 100 ns;
    I <= "1001";
    S <= "00";
    MSB <= '1';
    LSB <= '0';
    Reset <= '0';
    wait for 100 ns;
    I <= "1001";
    S <= "01";
    wait for 100 ns;
    I <= "1001";
    S <= "10";
    wait for 100 ns;
    I <= "1001";
    S <= "11";
    wait for 100 ns;
    I <= "1100";
    S <= "00";
    wait for 100 ns;
    I <= "1100";
    S <= "01";
    wait for 100 ns;
    I <= "1100";
    S <= "10";
    wait for 100 ns;
    I <= "1100";
    S <= "11";

    wait;
end process;

```

Test Bench Result:

 

1.B) UpDown Counter

Circuit Diagram



VHDL Implementation:

```
entity UpDownCounter is
    Port ( Up : in  STD_LOGIC;
          Down : in  STD_LOGIC;
          Clock : in  STD_LOGIC;
          Reset : in  STD_LOGIC;
          O : out  STD_LOGIC_VECTOR (3
downto 0));
end UpDownCounter;

architecture Behavioral of UpDownCounter
is
    component DFlipFlop
        Port ( D : in  STD_LOGIC;
              Reset : in  STD_LOGIC;
              Clock : in  STD_LOGIC;
              Q : out  STD_LOGIC;
              Qn : out  STD_LOGIC);
    end component;

    signal A : STD_LOGIC_VECTOR (3 downto
0);
    signal B : STD_LOGIC_VECTOR (3 downto
0);
    signal C : STD_LOGIC_VECTOR (6 downto
0);
    signal F : STD_LOGIC_VECTOR (3 downto
0);
    signal K : STD_LOGIC_VECTOR (3 downto
0);
begin
```

```
C(0) <= (not Up) and Down ;
K(0) <= Up or C(0);
F(0) <= K(0) xor A(0);
FF0 : DFlipFlop port map
(F(0),Reset,Clock,A(0),B(0));


C(1) <= C(0) and B(0);
C(2) <= Up and A(0);
K(1) <= C(1) or C(2);
F(1) <= K(1) xor A(1);
FF1 : DFlipFlop port map
(F(1),Reset,Clock,A(1),B(1));

C(3) <= C(1) and B(1);
C(4) <= C(2) and A(1);
K(2) <= C(3) or C(4);
F(2) <= K(2) xor A(2);
FF2 : DFlipFlop port map
(F(2),Reset,Clock,A(2),B(2));

C(5) <= C(3) and B(2);
C(6) <= C(4) and A(2);
K(3) <= C(5) or C(6);
F(3) <= K(3) xor A(3);
FF3 : DFlipFlop port map
(F(3),Reset,Clock,A(3),B(3));

O(0) <= A(0);
O(1) <= A(1);
O(2) <= A(2);
O(3) <= A(3);
end Behavioral;
```

RTL Schematic:

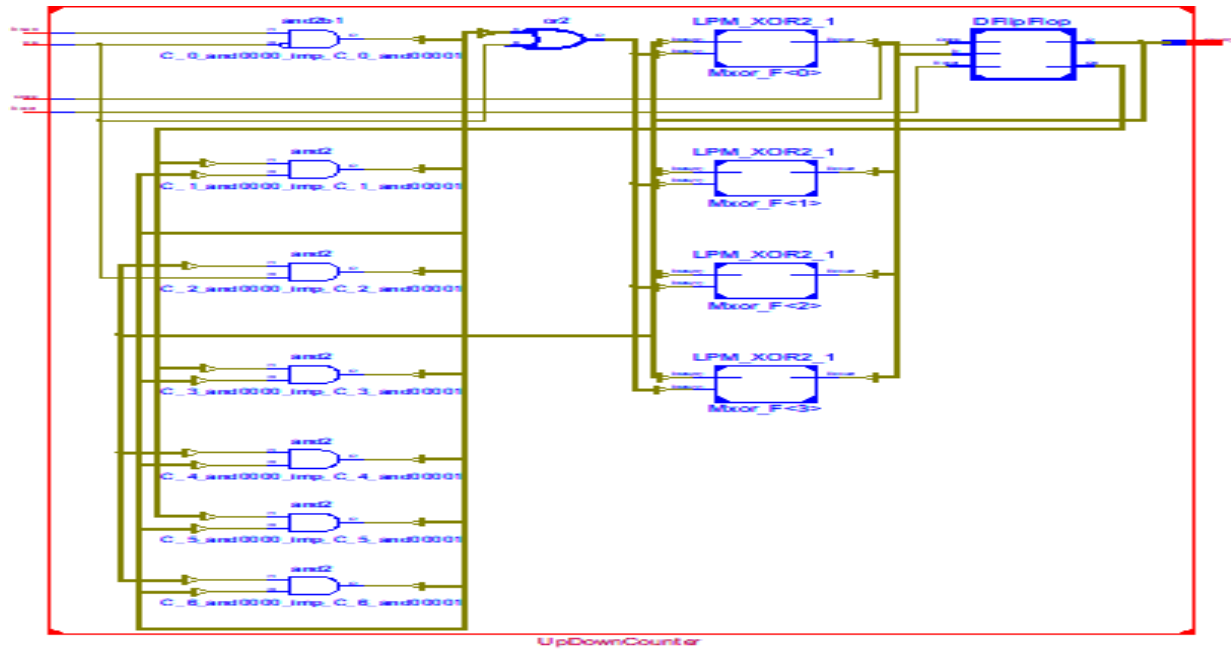

Test Bench Input:

```

signal Up : std_logic := '0';
signal Down : std_logic := '0';
signal Clock : std_logic := '0';
signal Reset : std_logic := '1';

signal O : std_logic_vector(3 downto
0);

constant Clock_period : time := 100
ns;

Clock_process : process
begin
    Clock <= '0';
    wait for Clock_period/2;
    Clock <= '1';
    wait for Clock_period/2;
end process;


```

```

stim_proc: process
begin
    Reset <= '1';
    wait for 100 ns;
    Up <= '1';
    Reset <= '0';
    wait for 100 ns;
    Up <= '1';
    wait for 100 ns;
    Up <= '1';
    wait for 100 ns;
    Up <= '1';
    wait for 100 ns;
    Up <= '0';
    Down <= '1';
    wait for 100 ns;
    Up <= '0';
    Down <= '1';
    wait for 100 ns;
    Up <= '0';
    Down <= '1';
    wait for 100 ns;
    Up <= '0';
    Down <= '1';
    wait;
end process;

```

Test Bench Result:

 

1.C) Johnson Counter

Circuit Diagram



VHDL Implementation

```
entity JohnsonCounter is
    Port ( Clock : in  STD_LOGIC;
          Reset : in  STD_LOGIC;
          O : out  STD_LOGIC_VECTOR (3
downto 0));
end JohnsonCounter;

architecture Behavioral of
JohnsonCounter is

component TFlipFlop
    Port ( T : in  STD_LOGIC;
          Reset : in  STD_LOGIC;
          Clock : in  STD_LOGIC;
          Q : out  STD_LOGIC;
          Qn : out  STD_LOGIC);
end component;

signal A : STD_LOGIC_VECTOR (3 downto
0);
signal B : STD_LOGIC_VECTOR (3 downto
0);
signal C : STD_LOGIC_VECTOR (3 downto
0);
```

```
begin

C(0) <= B(3) xor A(0);
FF0 : TFlipFlop port
map(C(0),Reset,Clock,A(0),B(0));

C(1) <= A(1) xor A(0);
FF1 : TFlipFlop port
map(C(1),Reset,Clock,A(1),B(1));


C(2) <= A(2) xor A(1);
FF2 : TFlipFlop port
map(C(2),Reset,Clock,A(2),B(2));

C(3) <= A(3) xor A(2);
FF3 : TFlipFlop port
map(C(3),Reset,Clock,A(3),B(3));

O(0) <= A(3);
O(1) <= A(2);
O(2) <= A(1);
O(3) <= A(0);

end Behavioral;
```

RTL Schematic:

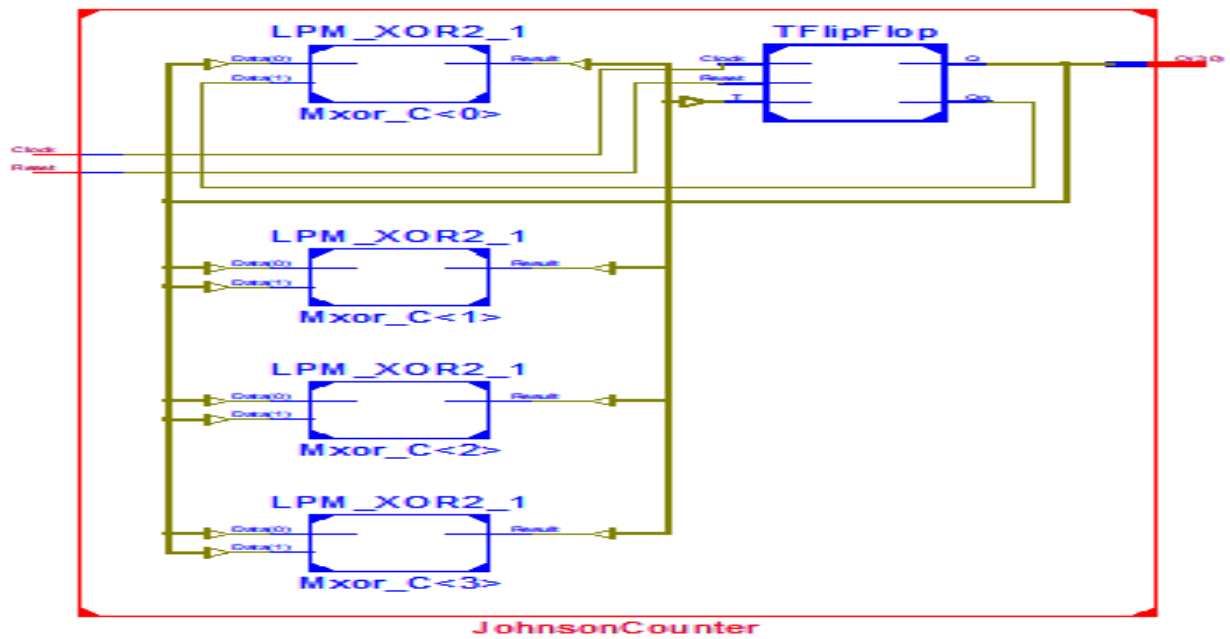

Test Bench Input:

```

signal Clock : std_logic := '0';
signal Reset : std_logic := '1';

signal O : std_logic_vector(3 downto 0);


constant Clock_period : time := 100 ns;

Clock_process : process
begin
    Clock <= '0';
    wait for Clock_period/2;
    Clock <= '1';
    wait for Clock_period/2;
end process;

stim_proc: process
begin
    Reset <= '1';
    wait for 100 ns;
    Reset <= '0';
    wait;
end process;


END;
```

Test Bench Result:

 

1.D) Asynchronous Binary Ripple Counter

Circuit Diagram

 

VHDL Implementation:

```
entity AsynchronousBRC is
    Port ( Clock : in  STD_LOGIC;
          Reset : in  STD_LOGIC;
          O : out  STD_LOGIC_VECTOR (3
downto 0));
end AsynchronousBRC;

architecture Behavioral of
AsynchronousBRC is

component JKFlipFlop
    Port ( J : in  STD_LOGIC;
          K : in  STD_LOGIC;
          Reset : in  STD_LOGIC;
          Clock : in  STD_LOGIC;
          Q : out  STD_LOGIC;
          Qn : out  STD_LOGIC);
end component;

signal A : STD_LOGIC_VECTOR (3 downto
0);
signal B : STD_LOGIC_VECTOR (3 downto
0);
```

```
begin

FF0 : JKFlipFlop port map
(B(0),A(0),Reset,Clock,A(0),B(0));

FF1 : JKFlipFlop port map
(B(1),A(1),Reset,not A(0),A(1),B(1));


FF2 : JKFlipFlop port map
(B(2),A(2),Reset,not A(1),A(2),B(2));

FF3 : JKFlipFlop port map
(B(3),A(3),Reset,not A(2),A(3),B(3));

O(0) <= A(0);
O(1) <= A(1);
O(2) <= A(2);
O(3) <= A(3);

end Behavioral;
```


RTL Schematic:

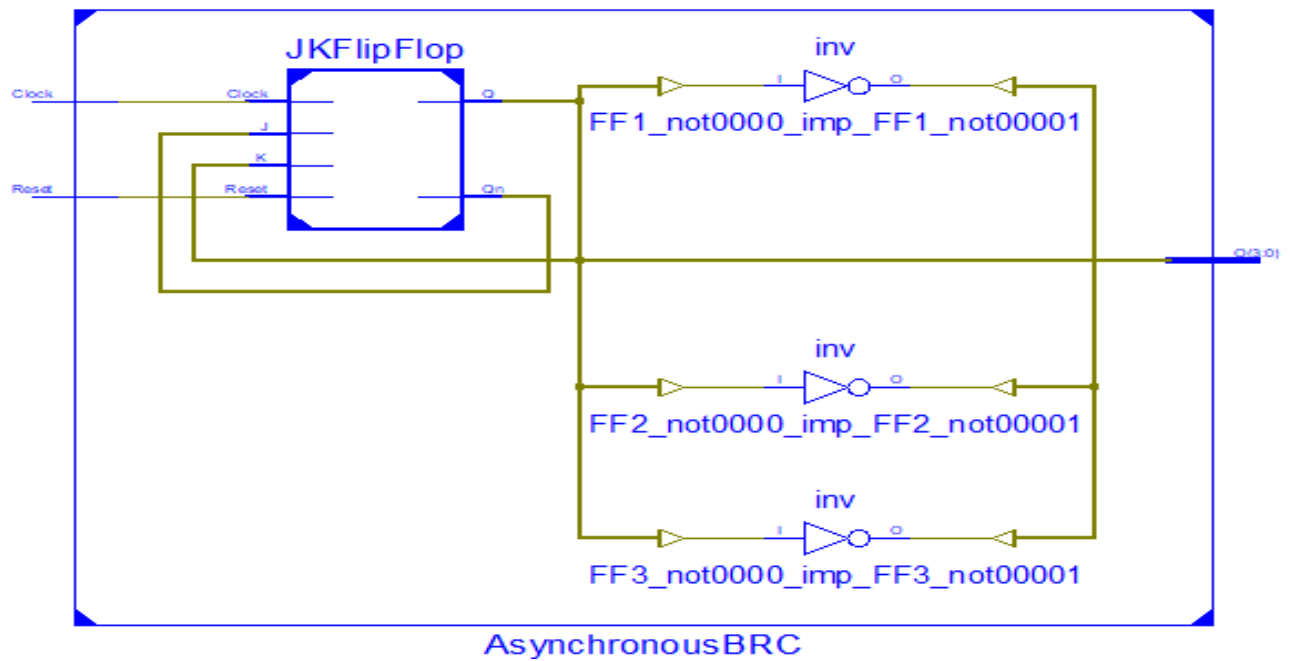

Test Bench Input:

```

signal Clock : std_logic := '0';
signal Reset : std_logic := '1';


signal O : std_logic_vector(3 downto 0);

constant Clock_period : time := 100 ns;

Clock_process : process
begin
    Clock <= '0';
    wait for Clock_period/2;
    Clock <= '1';
    wait for Clock_period/2;
end process;

stim_proc: process
begin
    Reset <= '1';
    wait for 100 ns;
    Reset <= '0';
    wait;
end process;
END;
```

Test Bench Result:

 

2.) Binary Divider

Circuit Diagram



VHDL Implementation:

```
entity BinaryDivider is
    Port ( A : in  STD_LOGIC_VECTOR (3
downto 0);
         B : in  STD_LOGIC_VECTOR (3
downto 0);
         SM: in  STD_LOGIC;
         Clock : in  STD_LOGIC;
         Reset : in  STD_LOGIC;
         Q : out  STD_LOGIC_VECTOR (3
downto 0);
         R : out  STD_LOGIC_VECTOR (3
downto 0));
end BinaryDivider;

architecture Behavioral of BinaryDivider
is
    component UpDownCounter
        Port ( Up : in  STD_LOGIC;
              Down : in  STD_LOGIC;
              Clock : in  STD_LOGIC;
              Reset : in  STD_LOGIC;
              O : out  STD_LOGIC_VECTOR (3
downto 0));
    end component;
```

```
    component FourBitSubtractor
        Port ( A : in  STD_LOGIC_VECTOR (3
downto 0);
              B : in  STD_LOGIC_VECTOR (3
downto 0);
              S : out  STD_LOGIC_VECTOR
(3 downto 0);
              C : out  STD_LOGIC);
    end component;

    component FourBitRegister
        Port ( I : in  STD_LOGIC_VECTOR (3
downto 0);
              SE : in  STD_LOGIC;
              L : in  STD_LOGIC_VECTOR
(3 downto 0);
              Clock : in  STD_LOGIC;
              Reset : in  STD_LOGIC;
              O : out  STD_LOGIC_VECTOR
(3 downto 0));
    end component;
```

```

component FourBitComparator
  Port ( a : in  STD_LOGIC_VECTOR (3
downto 0);
        b : in  STD_LOGIC_VECTOR (3
downto 0);
        g : out  STD_LOGIC;
        e : out  STD_LOGIC;
        l : out  STD_LOGIC);
end component;

signal GR,EQ,LE : STD_LOGIC;
signal RA : STD_LOGIC_VECTOR (3 downto
0);
signal QAB : STD_LOGIC_VECTOR (3 downto
0);
signal Cl : STD_LOGIC ;
signal x : STD_LOGIC ;

```

```

begin

COM : FourBitComparator port
map (RA,B,GR,EQ,LE) ;
Cl <= (not LE) and Clock ;

COUN : UpDownCounter port
map ('1','0',Cl,Reset,Q) ;

REG : FourBitRegister port
map (A,SM,QAB,Clock,Reset,RA) ;


SUBS : FourBitSubtractor port
map (RA,B,QAB,x) ;

R <= RA ;

end Behavioral;

```

RTL Schematic:

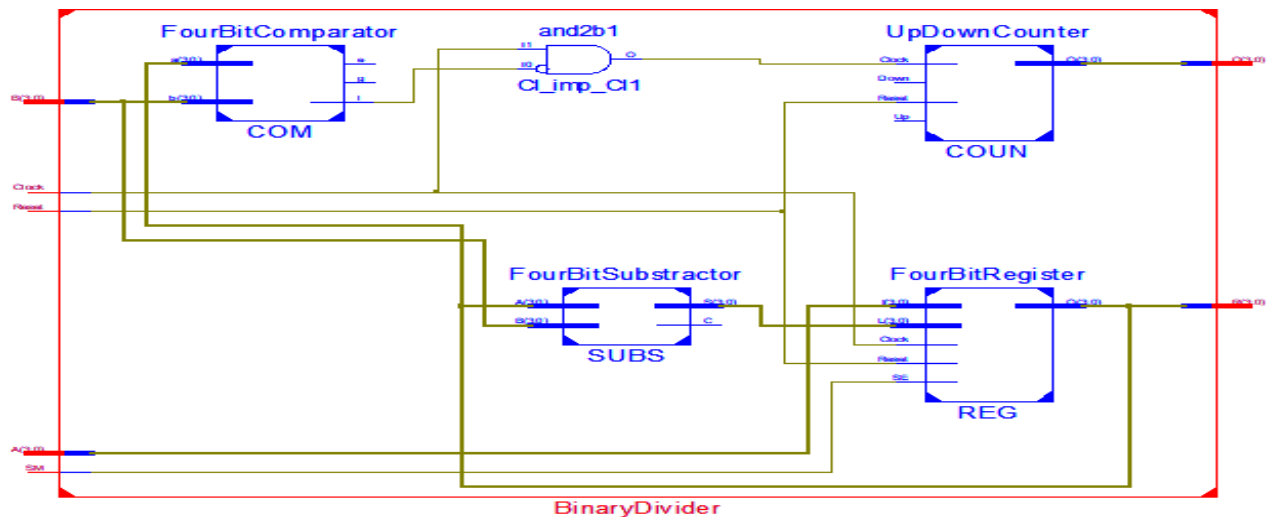

Test Bench Input:

```

signal A : std_logic_vector(3 downto 0)
:= (others => '0');
signal B : std_logic_vector(3 downto 0)
:= (others => '0');
signal SM : std_logic := '0';
signal Clock : std_logic := '1';
signal Reset : std_logic := '1';

signal Q : std_logic_vector(3 downto 0);
signal R : std_logic_vector(3 downto 0);

constant Clock_period : time := 100
ns;

Clock_process :process
begin
    Clock <= '0';
    wait for Clock_period/2;
    Clock <= '1';
    wait for Clock_period/2;
end process;

```

```

stim_proc: process
begin

    A <= "1001";
    Reset <= '1';
    SM <= '1';
    wait for 100 ns;
    A <= "1001";
    B <= "0010";
    Reset <= '0';


    wait for 100 ns ;
    SM <= '0';

    wait;
end process;

END;

```

Test Bench Result:

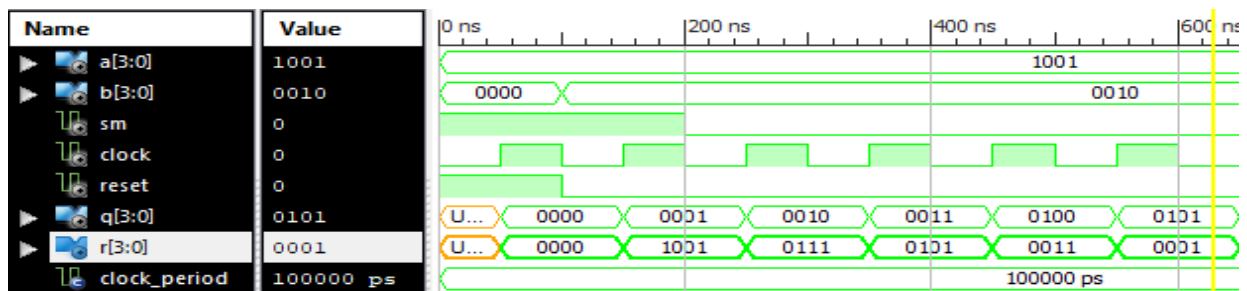

4.A) Simple Binary Cell

Circuit Diagram

VHDL Implementation:

```
entity BinaryCell is
    Port ( I : in  STD_LOGIC;
          S : in  STD_LOGIC;
          RW : in  STD_LOGIC;
          O : out  STD_LOGIC);
end BinaryCell;

architecture Behavioral of BinaryCell is

    component SRLatch
        Port ( S : in  STD_LOGIC;
              R : in  STD_LOGIC;
              E : in  STD_LOGIC;
              Q : out  STD_LOGIC;
              Qn : out  STD_LOGIC);
    end component;
```

```
    signal S1 : STD_LOGIC;
    signal R1 : STD_LOGIC;
    signal Q1,Qn1 : STD_LOGIC;


    begin
        S1 <= I and (not RW) and S ;
        R1 <= (not I) and (not RW) and S ;

        LA : SRLatch port map(S1,R1,S,Q1,Qn1);

        O <= S and Q1 and RW ;

    end Behavioral;
```


RTL Schematic :

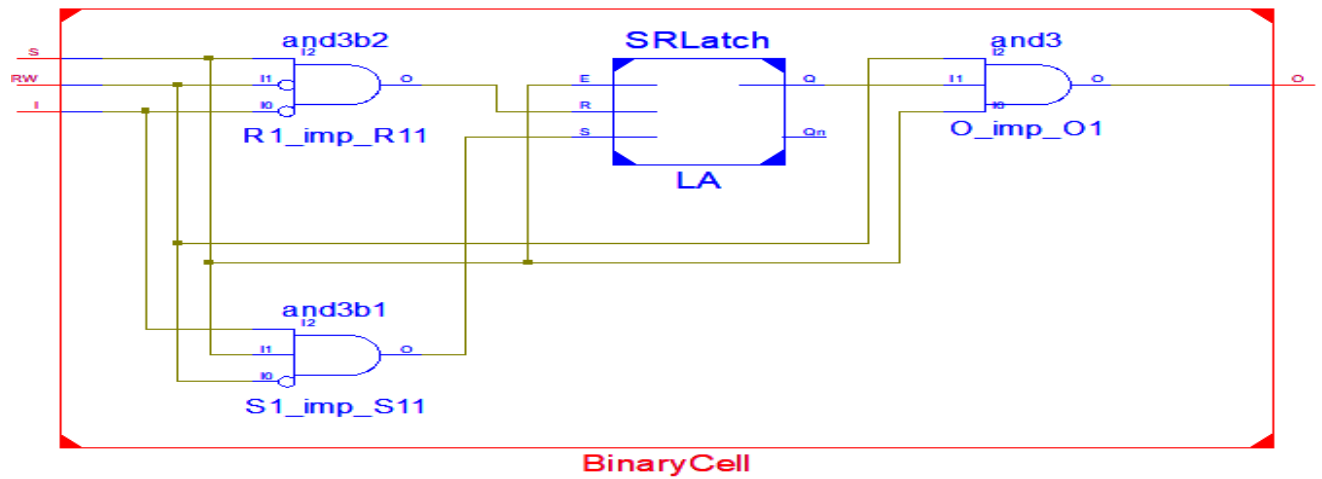

Test Bench Input:

<pre> stim_proc: process begin I <= '0'; S <= '1'; RW <= '0'; wait for 100 ns; I <= '1'; S <= '0'; RW <= '0'; wait for 100 ns; I <= '1'; S <= '1'; RW <= '1'; wait for 100 ns; I <= '1'; S <= '1'; RW <= '0'; </pre>	<pre> wait for 100 ns; I <= '1'; S <= '1'; RW <= '1'; wait for 100 ns; I <= '0'; S <= '0'; RW <= '0'; wait for 100 ns; I <= '1'; S <= '1'; RW <= '1'; wait; end process; END; </pre>
--	---

Test Bench Result:

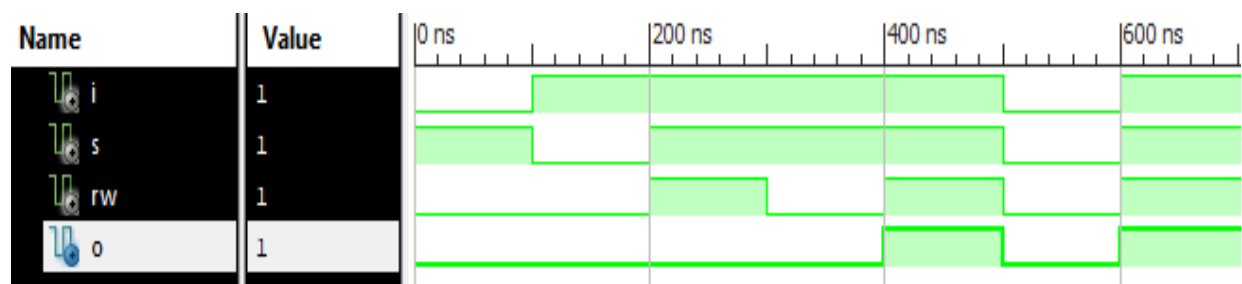

4.B) 4X4 RAM


Circuit Diagram



VHDL Implementation:

<pre>entity RAM is Port (I : in STD_LOGIC_VECTOR (3 downto 0)); AI : in STD_LOGIC_VECTOR (1 downto 0); O : out STD_LOGIC_VECTOR (3 downto 0); En : in STD_LOGIC; RW : in STD_LOGIC); end RAM; architecture Behavioral of RAM is component DECO Port (A : in STD_LOGIC; B : in STD_LOGIC; E : in STD_LOGIC; D : out STD_LOGIC_VECTOR (3 downto 0)); end component; component BinaryCell Port (I : in STD_LOGIC; S : in STD_LOGIC; RW : in STD_LOGIC; O : out STD_LOGIC); end component; signal W :STD_LOGIC_VECTOR (3 downto 0); signal T :STD_LOGIC_VECTOR (15 downto 0);</pre>	<pre>begin DE : DECO port map(AI(1),AI(0),En,W); BC0 : BinaryCell portmap(I(3),W(0),RW,T(0)); BC1 : BinaryCell portmap(I(2),W(0),RW,T(1)); BC2 : BinaryCell portmap(I(1),W(0),RW,T(2)); BC3 : BinaryCell portmap(I(0),W(0),RW,T(3)); BC4 : BinaryCell portmap(I(3),W(1),RW,T(4)); BC5 : BinaryCell portmap(I(2),W(1),RW,T(5)); BC6 : BinaryCell portmap(I(1),W(1),RW,T(6)); BC7 : BinaryCell portmap(I(0),W(1),RW,T(7)); BC8 : BinaryCell portmap(I(3),W(2),RW,T(8)); BC9 : BinaryCell portmap(I(2),W(2),RW,T(9)); BC10 : BinaryCell port map(I(1),W(2),RW,T(10)); BC11 : BinaryCell port map(I(0),W(2),RW,T(11)); BC12 : BinaryCell port map(I(3),W(3),RW,T(12)); BC13 : BinaryCell port map(I(2),W(3),RW,T(13)); BC14 : BinaryCell port map(I(1),W(3),RW,T(14)); BC15 : BinaryCell port map(I(0),W(3),RW,T(15)); O(3) <= T(0) or T(4) or T(8) or T(12); O(2) <= T(1) or T(5) or T(9) or T(13); O(1) <= T(2) or T(6) or T(10) or T(14); O(0) <= T(3) or T(7) or T(11) or T(15); end Behavioral;</pre>
---	---

RTL Schematic :

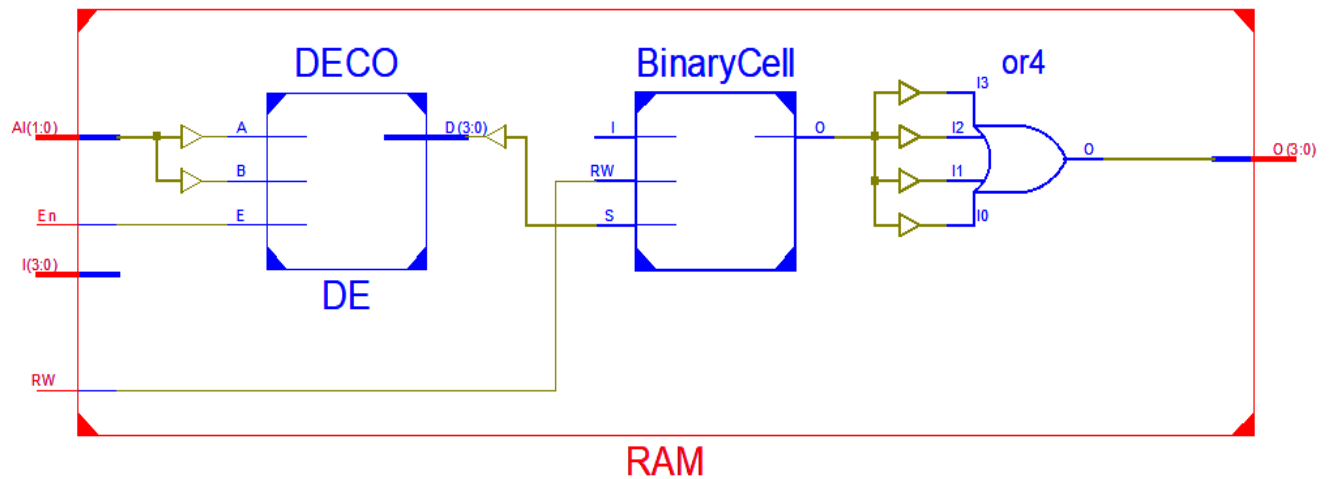

Test Bench Input:


```

stim_proc: process
begin
    I <= "0000";
    AI <= "00";
    En <= '1';
    RW <= '0';
    wait for 100 ns;
    AI <= "01";
    I <= "0001";
    wait for 100 ns;
    AI <= "10";
    I <= "0010";
    wait for 100 ns;
    AI <= "11";
    I <= "1001";
    wait for 100 ns;
    RW <= '1';
    AI <= "10";
    wait for 100 ns;
    AI <= "00";
    wait for 100 ns;
    AI <= "01";


    wait for 100 ns;
    AI <= "11";
    wait for 100 ns;
    AI <= "10";
    wait for 100 ns;
    AI <= "00";
    wait for 100 ns;
    AI <= "01";

    wait;
end process;
END;
```

Test Bench Result:

 

5.) Circuit Diagram

 

VHDL Implementation:

```

entity ROM is
    Port ( I : in  STD_LOGIC_VECTOR (2 downto
0));
        O : out  STD_LOGIC_VECTOR (5 downto
0));
end ROM;

architecture Behavioral of ROM is

component DECODER
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          C : in  STD_LOGIC;
          D : out  STD_LOGIC_VECTOR (7 downto
0));
end component;

```

```

signal R : STD_LOGIC_VECTOR (7 downto 0);

begin


DEC : DECODER port map(I(2),I(1),I(0),R);

O(0) <= R(1) or R(3) or R(5) or R(7);
O(1) <= '0';
O(2) <= R(2) or R(6);
O(3) <= R(3) or R(5);
O(4) <= R(4) or R(5) or R(7);
O(5) <= R(6) or R(7);

end Behavioral;

```

RTL Schematic:

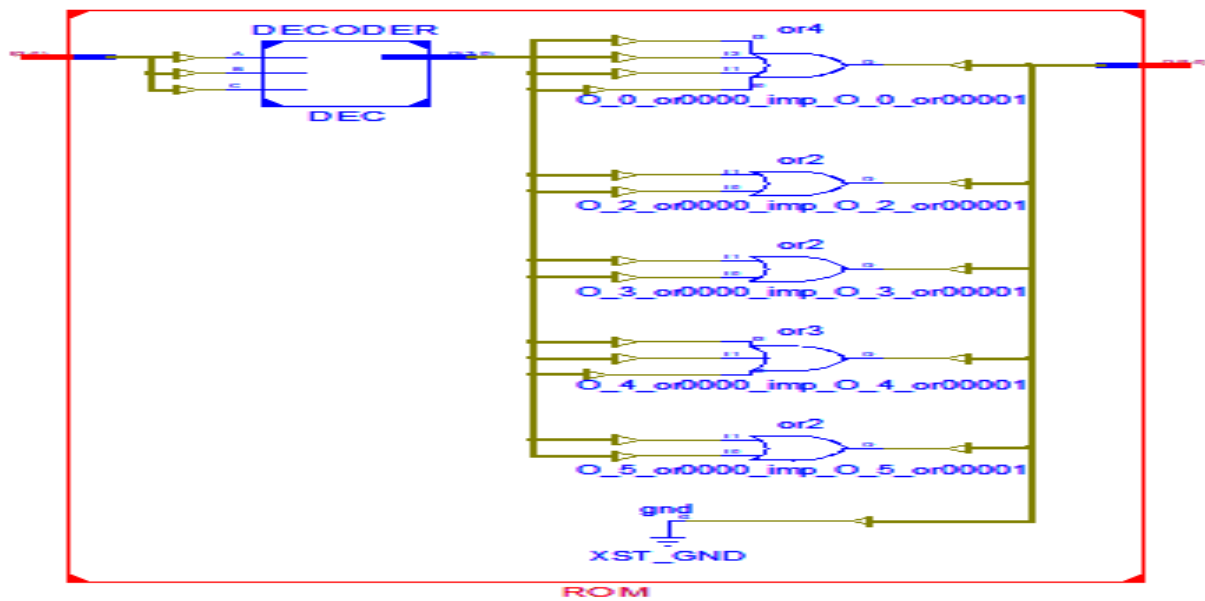

Test Bench Inputs :

```

stim_proc: process
begin
    I <= "000";
    wait for 100 ns;
    I <= "001";
    wait for 100 ns;
    I <= "010";
    wait for 100 ns;
    I <= "011";
    wait for 100 ns;
    I <= "100";

```

```

    wait for 100 ns;
    I <= "101";
    wait for 100 ns;
    I <= "110";
    wait for 100 ns;
    I <= "111";

```

```

    wait;
end process;

```

```

END;

```

Test Bench Results :

