



HACETTEPE UNIVERSITY
ELECTRICAL AND ELECTRONICS ENGINEERING
ELE419 – INTEGRATED CIRCUIT DESIGN
PROJECT REPORT
2021-2022 FALL

4 BIT ALU DESIGN USING 180nm CMOS TECHNOLOGY

Egemen Can AYDUĞAN - 21728036

I. INTRODUCTION

I design a 4-bit arithmetic and logic unit (ALU) in CMOS technology in this project. I use ELECTRIC VLSI for layout design, and also use LTspice simulation program to obtain input-output characteristics of the ALU.

First of all, I will explain the operations that our ALU can do and the operation codes (Op-Code) that indicate the operations to be performed. After that, 4-bit ALU schematic and its components are explained respectively. Then, VLSI layout and its simulation are shown for each part respectively. Finally, the report is finished with “Conclusion” and “References” parts.

II. CIRCUIT DESIGN

In computing, an arithmetic logic unit (ALU) is a combinational digital circuit that performs arithmetic and bitwise operations on integer binary numbers.

I designed a 4-bit ALU with eight processes. I used a 3 bit bus to select the process. Table 1 shows the opcodes and related operations of the ALU.

OP-CODE			OPERATION
C ₂	C ₁	C ₀	
0	0	0	A AND B
0	0	1	A XOR B
0	1	0	A OR B
0	1	1	NOT A
1	0	0	A + B
1	0	1	A – B
1	1	0	A + 1
1	1	1	A – 1

Table 1 : Opcodes of the ALU

I did not choose these opcodes randomly. The C₂, determines whether the operation is arithmetic or logic.

For logic operations, the C₁ and C₀ are designed to do what logic operation. All of them have A input for arithmetic operations. B or 1 will come depending on what I'm going to do. For arithmetic operations, C₁ whether the addition/subtraction is done with the value 1 or B. And C₀ determines whether the operation is addition or subtraction.

 


Fig.1 Block Diagram of 4 Bit ALU

The ALU consists of four blocks for 4 bits. Each block has a block for doing arithmetic operations and a block for doing logical operations. Each block consists of 6 inputs and 2 outputs. Inputs 2 of which are processed inputs A and B. The other 3 inputs are opcodes(C_0, C_1, C_2) and the last input is the C_{in} input. We do not define C_{in} in the Spice Code because Initial C_{in} takes the value of C_0 . Outputs are Out and CarryOut. Output is the result bit of the operations, CarryOut is the bit that comes out after the arithmetic operations and is connected to the C_{in} of the next block.

Let's define the circuits in 4Bit ALU in order from smallest to largest.

- 2x1 MUX:

 


Fig.2 Logic Circuit of 2x1Mux

 


Fig.3 Layout of 2x1Mux

I used the 2x1Mux circuit in my arithmetic unit. Thanks to Mux, I am doing addition/subtraction with B or addition/subtraction with 1 in my arithmetic circuit. I designed the Opcode C_1 as the selected bit of the Mux circuit. If C_1 is 0 then my Full Adder is trading with B. If C_1 is 1, my Full Adder is trading with 1.

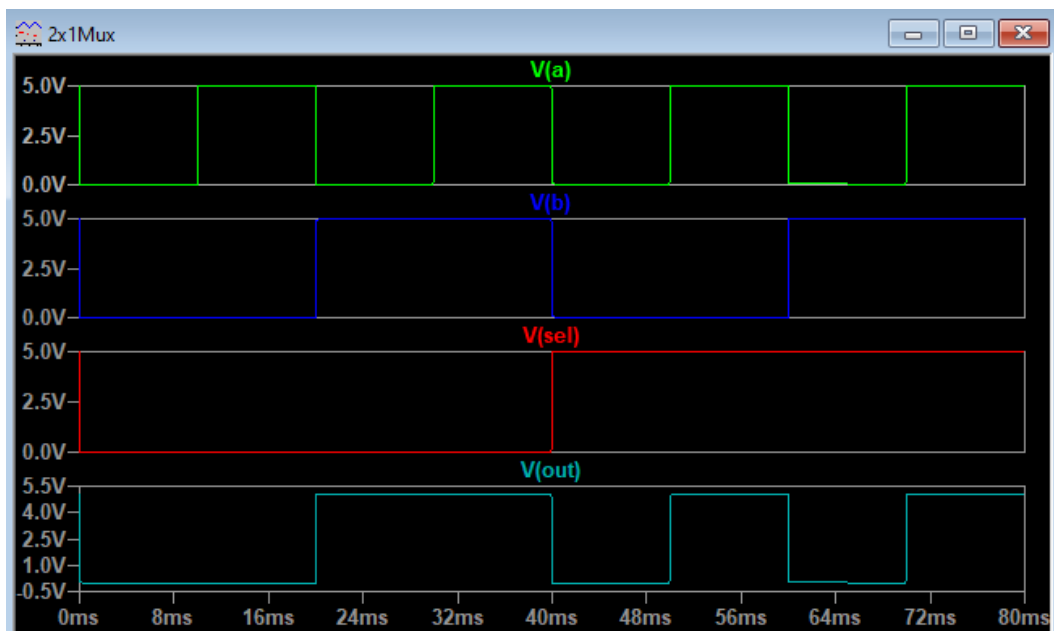


Fig.4 Simulation Results of 2x1Mux

- 2x4 DECODER:

 


Fig.5 Logic Circuit of 2x4 Decoder

 


Fig.6 Layout of 2x4 Decoder

I used my 2x4 Decoder to design my logic unit. I select my logic operations by connecting the C0 and C1 selection inputs to my decoder. The outputs in the decoder go to And, Xor, Or and Inverter operations, respectively.

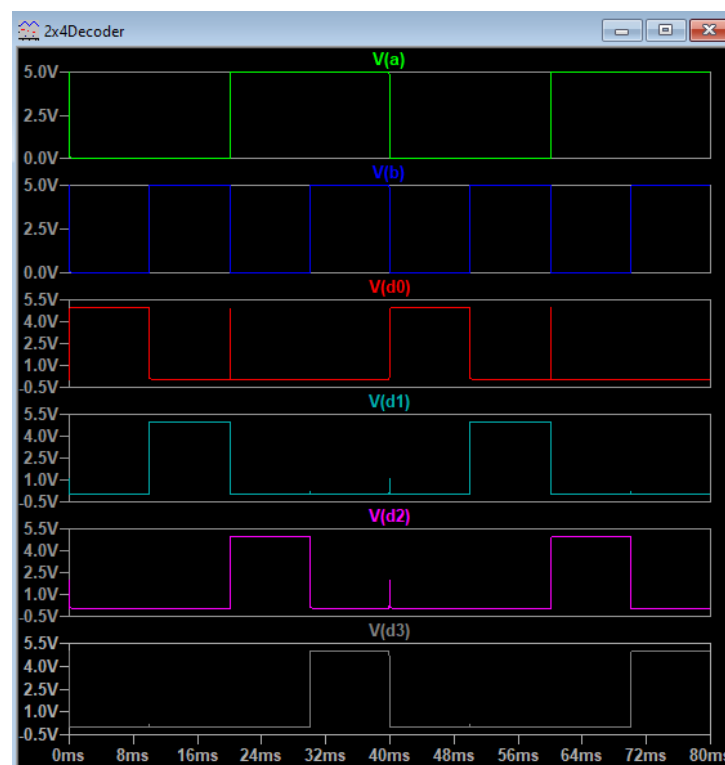


Fig.7 Simulation Results of 2x4Decoder

- FULL ADDER

 


Fig.8 Logic Circuit of Full Adder

 


Fig.9 Layout of Full Adder

I used my Full Adder to add or subtract in my arithmetic unit. It consists of 3 inputs(A,B,Cin) and 2 outputs(Sum,CarryOut). I decide the addition or subtraction process with the Cin input. CarryOut is linking to the next block as Cin.

 


Fig.10 Simulation Results of Full Adder

- LOGIC CIRCUITS IN THE LOGICAL UNIT

I made the logic circuits in my logic unit **with the select pin** because to reduce the area. One of the most important aspects of my project is area. Select Bit is the output bit from the 2x4Decoder.

 
 


Fig.11 Layout of AND Gate with Select Pin Fig.12 Simulation Results of AND Gate with Select Pin

 
 


Fig.13 Layout of XOR Gate with Select Pin Fig.14 Simulation Results of XOR Gate with Select Pin

 
 


Fig.15 Layout of OR Gate with Select Pin Fig.16 Simulation Results of OR Gate with Select Pin

 
 


Fig.17 Layout of Inverter with Select Pin Fig.18 Simulation Results of Inverter with Select Pin

- 4 ENTRY OR GATE

 


Fig.19 Layout of 4-Entry OR Gate

I used the 4-Entry OR Gate in my logical unit. I get the real result by inserting my outputs from And, Or, Xor and Inverter into the 4-Entry OR Gate. I put the output from here into the and gate with notC₂ and I get my logical output.

 


Fig.20 Simulation Results of 4-Entry OR Gate

- LOGICAL UNIT

 


Fig.21 Logic Circuit of Logical Unit

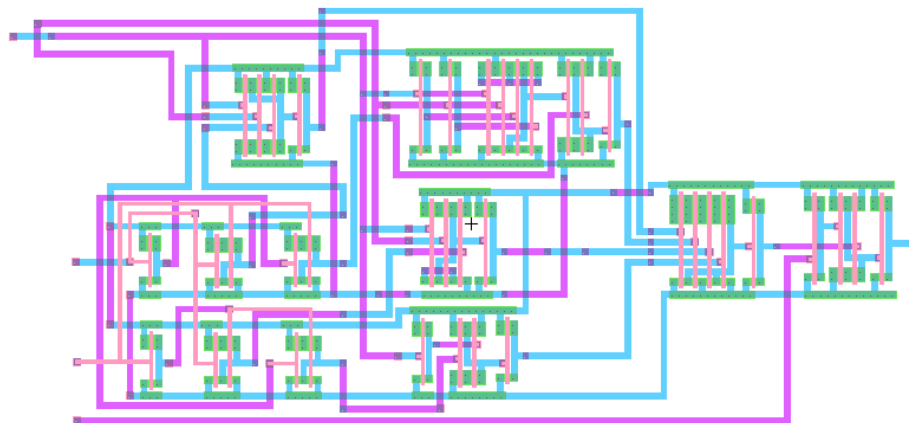


Fig.22 Layout of Logical Unit

 


Fig.23 Simulation Results of Logical Unit

C₀ = 0, C₁ = 0, C₂ = 0: 0ms-40ms AND Operation
 C₀ = 0, C₁ = 1, C₂ = 0: 40ms-80ms XOR Operation
 C₀ = 1, C₁ = 0, C₂ = 0: 80ms-120ms OR Operation
 C₀ = 1, C₁ = 1, C₂ = 0: 120ms-160ms NotA Operation
 C₂ must always be 0 for the Logic Unit to work. otherwise the result is always 0.

- ARITHMETIC UNIT

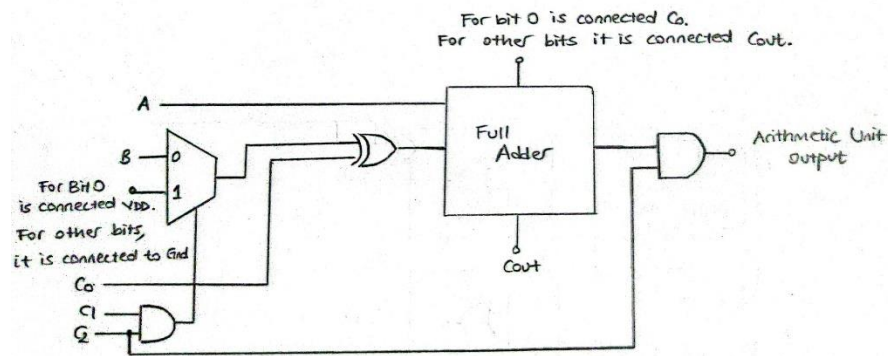


Fig.24 Logic Circuit of Arithmetic Unit

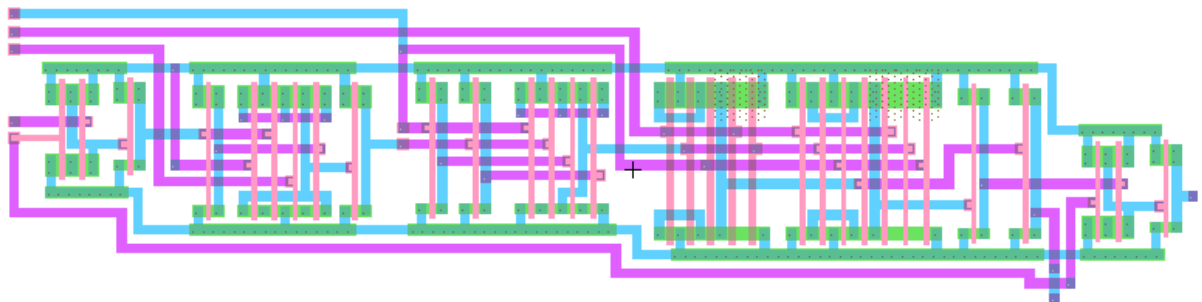


Fig.25 Layout of Arithmetic Unit

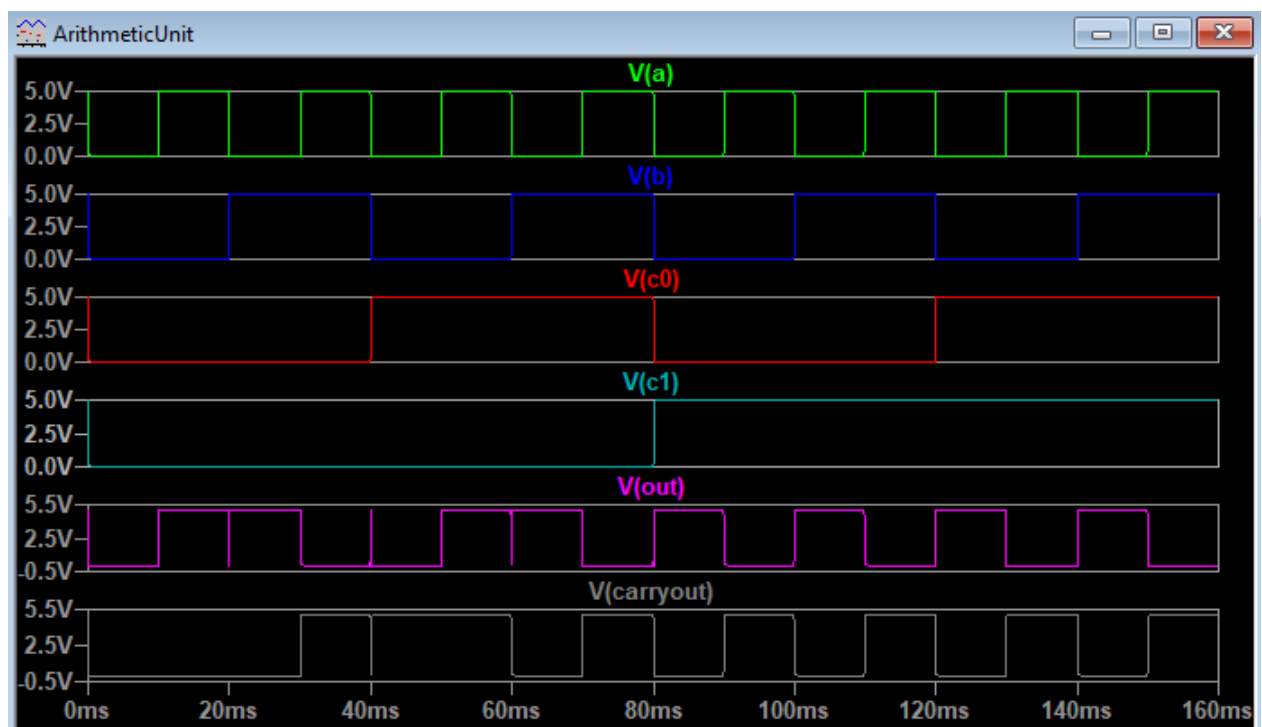


Fig.26 Simulation Results of Arithmetic Unit

$C_0 = 0, C_1 = 0, C_2 = 1$: 0ms-40ms A+B Operation
 $C_0 = 0, C_1 = 1, C_2 = 1$: 40ms-80ms A-B Operation
 $C_0 = 1, C_1 = 0, C_2 = 1$: 80ms-120ms A+1 Operation
 $C_0 = 1, C_1 = 1, C_2 = 1$: 120ms-160ms A-1 Operation
 C_2 must always be 1 for the Arithmetic Unit to work. otherwise the result is always 0.
 CarryOut output goes to the next block as Cin input.

- 1-Bit ALU

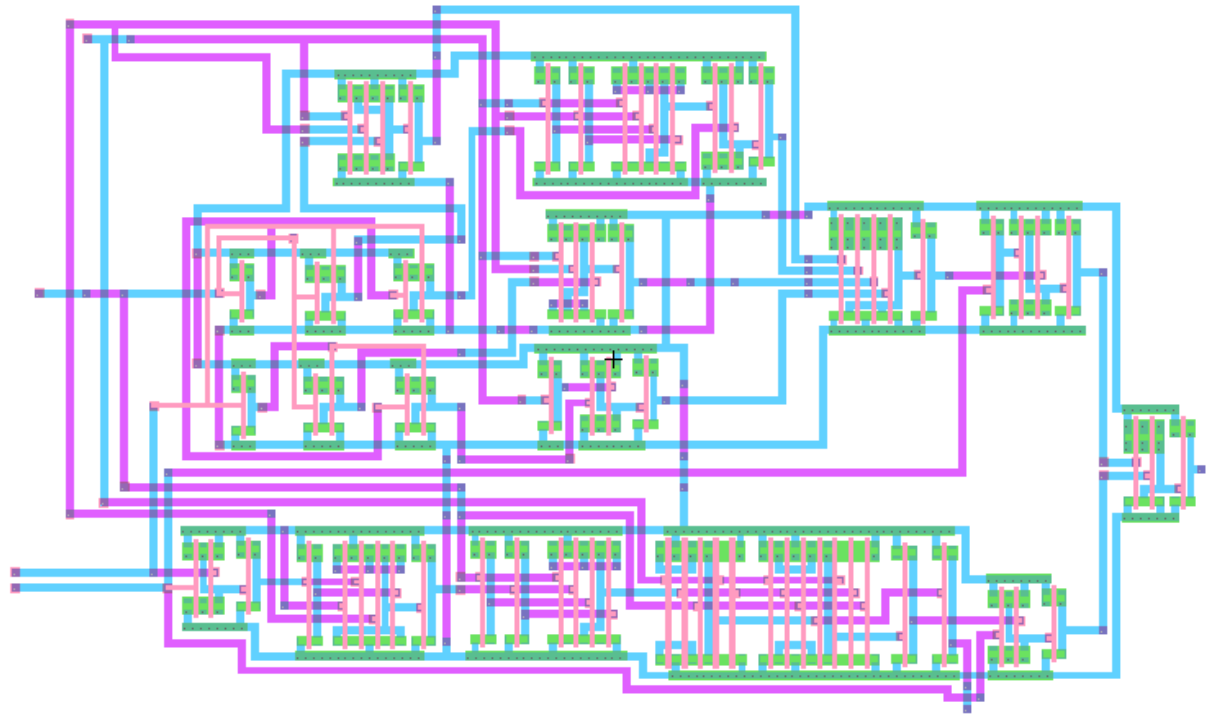


Fig.27 Layout of 1-Bit ALU

I connected the outputs of the arithmetical and logical unit to the 2-Entry OR Gate and designed my 1 Bit Alu. It works right.

When C2 is 0, it performs logical operations. When C1 is 1, it performs arithmetic operations.

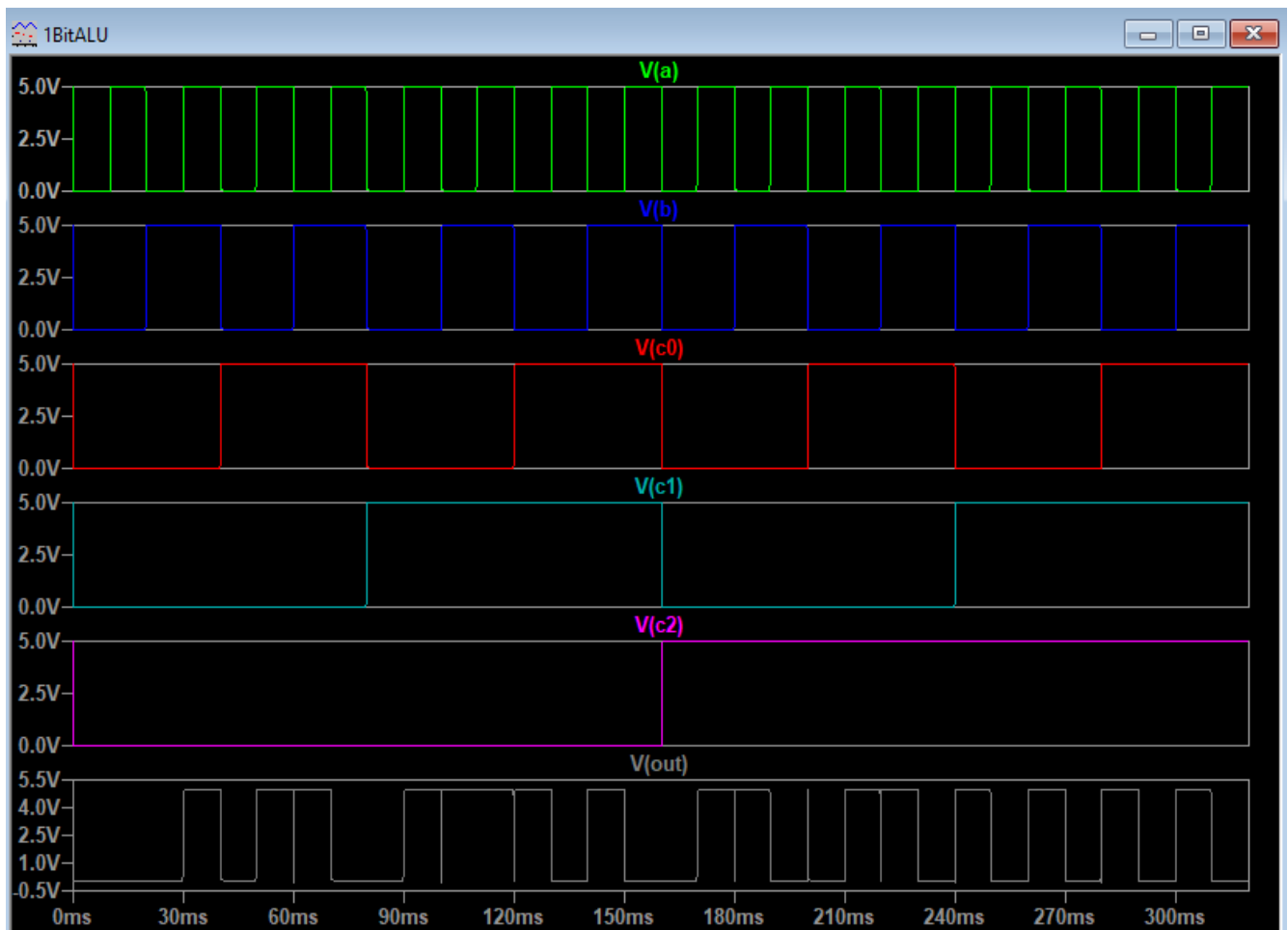


Fig.28 Simulation Results of 1-Bit ALU

III. FINAL DESIGN

4-Bit ALU Total Size: 837.5x1737

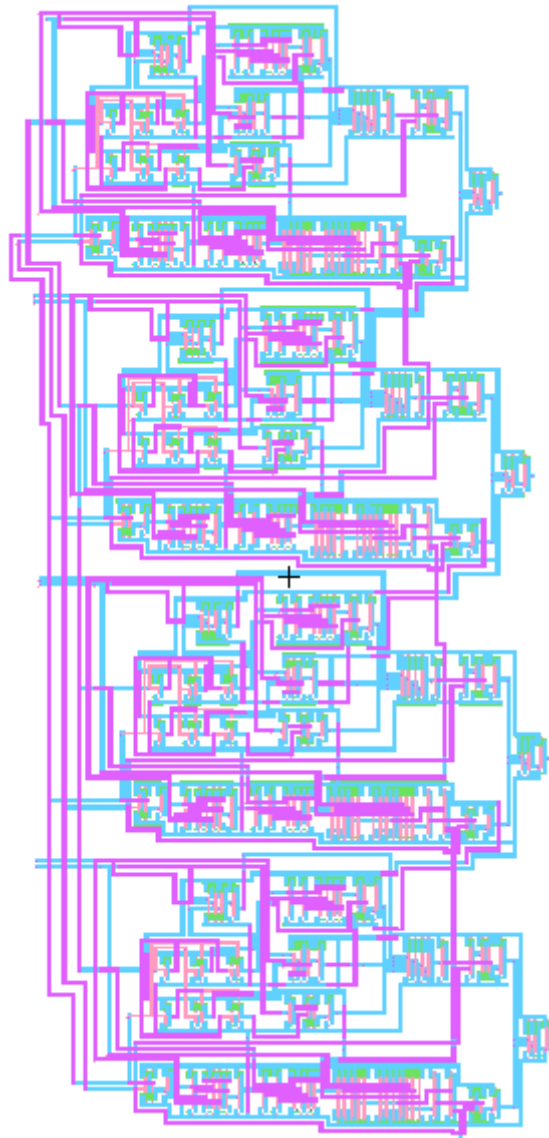


Fig.29 Layout of 4-Bit ALU

 


Fig.30 Simulation Results of AandB Operation

 


Fig.31 Simulation Results of AxorB Operation

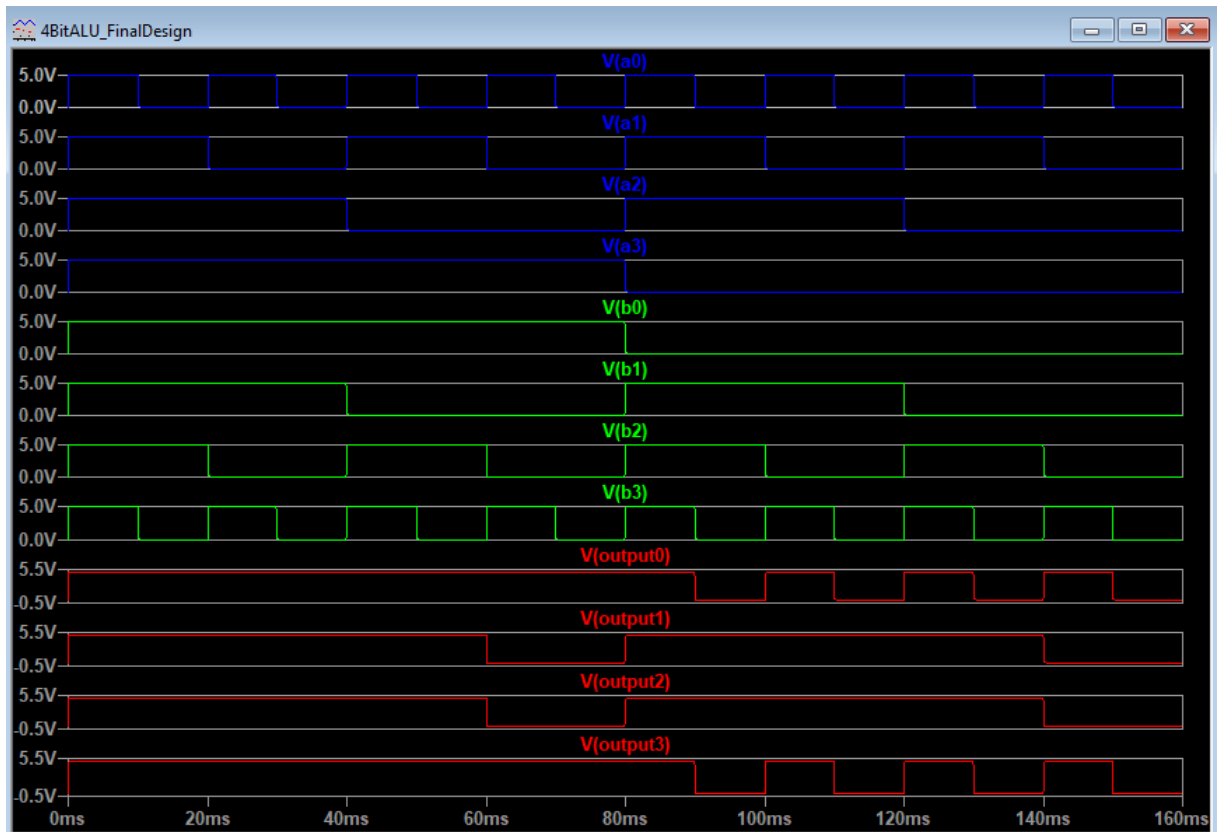


Fig.32 Simulation Results of AorB Operation

 


Fig.33 Simulation Results of notA Operation

 


Fig.34 Simulation Results of A+B Operation

 


Fig.35 Simulation Results of A-B Operation

 


Fig.36 Simulation Results of A+1 Operation

 


Fig.37 Simulation Results of A-1 Operation

IV. CONCLUSION

The layout of each part is simulated by using LTspice and input and output graphs are observed for all possible input. All layouts are working correctly. Then 4-bit ALU is checked for different inputs. I observe that the 4-bit ALU gives correct outputs.

REFERENCES

- Associate Profesör Dinçer Gökçen, ELE419 Integrated Circuit Design, Lecture Notes – Digital IC Design, Hacettepe University
- Neil H. E. Weste, David Money Harris, 2011, CMOS VLSI DESIGN A Circuit and System Perspective 4th Edition, Boston, Massachusetts
- M. Morris Mano, Michael D. Ciletti, 2013, Digital Design with an Introduction to the Verilog HDL 5th Edition, New Jersey
- R. Jacob Baker, 2019, CMOS Circuit Design, Layout and Simulation 4th Edition, New Jersey