



## ELE227 FUNDAMENTALS OF DIGITAL SYSTEM LABORATORY

### PRELIMINARY WORK-3

#### Student

Name: Egemen Can

Surname: Ayduđan

ID: 21728036

1.)

Circuit Diagram:

## VHDL Implementation

```

entity DECODER is
  Port ( A : in  STD_LOGIC;
        B : in  STD_LOGIC;
        C : in  STD_LOGIC;
        D : out STD_LOGIC_VECTOR (7
downto 0));
end DECODER;

architecture Behavioral of DECODER is

begin

D(0) <= (not A) and (not B) and (not C);
D(1) <= (not A) and (not B) and C;
D(2) <= (not A) and B and (not C);
D(3) <= (not A) and B and C;
D(4) <= A and (not B) and (not C);
D(5) <= A and (not B) and C;
D(6) <= A and B and (not C);
D(7) <= A and B and C;

end Behavioral;

```

```

entity FullSubtractorByDecoder is
  Port ( x : in  STD_LOGIC;
        y : in  STD_LOGIC;
        z : in  STD_LOGIC;
        Dif : out STD_LOGIC;
        Bor : out STD_LOGIC);
end FullSubtractorByDecoder;

architecture Behavioral of
FullSubtractorByDecoder is

component DECODER
  Port ( A : in  STD_LOGIC;
        B : in  STD_LOGIC;
        C : in  STD_LOGIC;
        D : out STD_LOGIC_VECTOR (7
downto 0));
end component;

signal T : STD_LOGIC_VECTOR (7 downto 0);

begin


Dec1 : DECODER port map(x,y,z,T(7 downto 0));

Dif <= T(1) or T(2) or T(4) or T(7);
Bor <= T(1) or T(2) or T(3) or T(7);

end Behavioral;

```


## RLT Schematic:

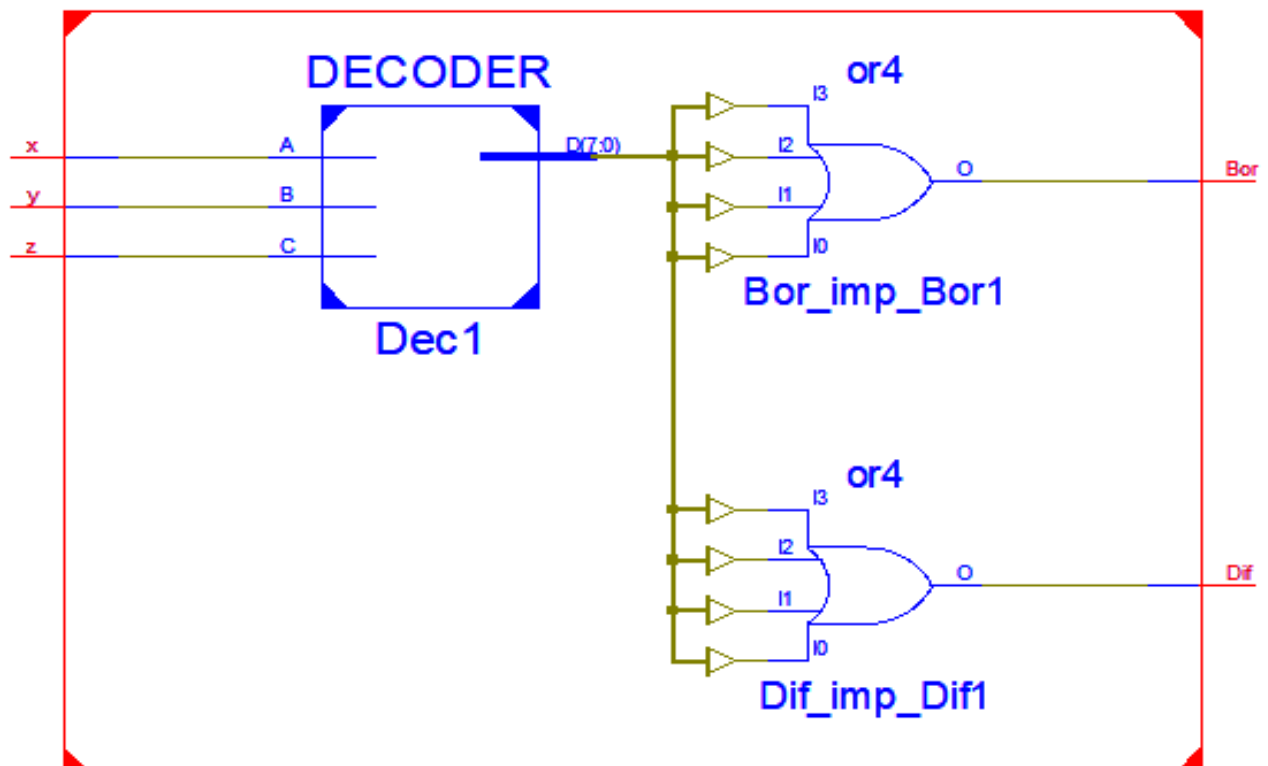

### TEST BENCH INPUT:


```
stim_proc: process
begin
    x <='0';
    y <='0';
    z <='0';
    wait for 100 ns;
    x <='0';
    y <='0';
    z <='1';
    wait for 100 ns;
    x <='0';
    y <='1';
    z <='0';
    wait for 100 ns;
    x <='0';
    y <='1';
    z <='1';
    wait for 100 ns;
    x <='1';
    y <='0';
    z <='0';
    wait for 100 ns;
    x <='1';
    y <='0';
    z <='1';
    wait for 100 ns;
    x <='1';
    y <='1';
    z <='0';
    wait for 100 ns;
    x <='1';
    y <='1';
    z <='1';
    wait;
end process;
```

### TEST BENCH RESULTS:

 

2.)

Circuit Diagram:

 

### VHDL Implementation


```
entity FourXOneMux is
  Port ( I : in  STD_LOGIC_VECTOR (3 downto 0);
         S : in  STD_LOGIC_VECTOR (1 downto 0);
         Y : out STD_LOGIC);
end FourXOneMux;

architecture Behavioral of FourXOneMux is
begin
  Y <= ((not S(1)) and (not S(0)) and I(0)) or
        ((not S(1)) and S(0) and I(1)) or
        (S(1) and (not S(0)) and I(2)) or
        (S(1) and S(0) and I(3));
end Behavioral;
```

```
entity Fonkby4x1Mux is
  Port ( x : in  STD_LOGIC;
         y : in  STD_LOGIC;
         z : in  STD_LOGIC;
         F : out STD_LOGIC);
end Fonkby4x1Mux;

architecture Behavioral of Fonkby4x1Mux is
  component FourXOneMux
    Port ( I : in  STD_LOGIC_VECTOR (3 downto 0);
          S : in  STD_LOGIC_VECTOR (1 downto 0);
          Y : out STD_LOGIC);
  end component;
  signal T : STD_LOGIC_VECTOR (3 downto 0);
  signal K : STD_LOGIC_VECTOR (1 downto 0);
begin
  T(0) <= '1';
  T(1) <= z;
  T(2) <= '1';
  T(3) <= '0';
  K(0) <= y;
  K(1) <= x;
  M1: FourXOneMux port map (T(3 downto 0),K(1
downto 0),F);
end Behavioral;
```

## RLT Schematic:

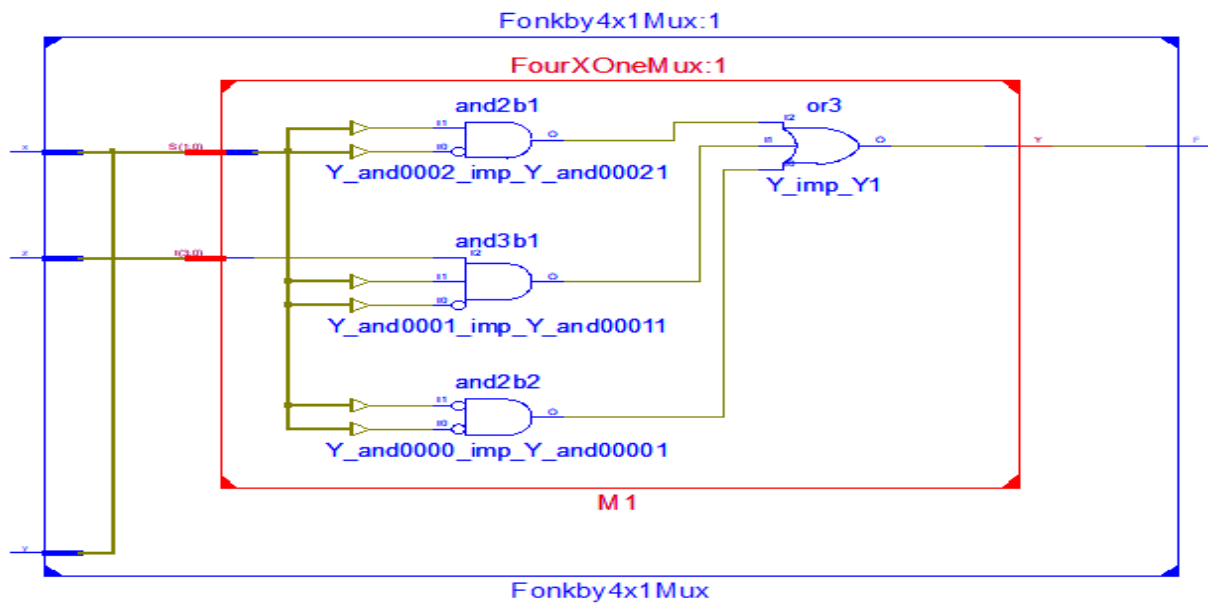


## TEST BENCH INPUT:

```
stim_proc: process
begin
    x<='0';
    y<='0';
    z<='0';
    wait for 100 ns;
    x<='0';
    y<='0';
    z<='1';
    wait for 100 ns;
    x<='0';
    y<='1';
    z<='0';
    wait for 100 ns;
    x<='0';
    y<='1';
    z<='1';
    wait for 100 ns;
    x<='1';
    y<='0';
    z<='0';
    wait for 100 ns;
    x<='1';
    y<='0';
    z<='1';
    wait for 100 ns;
    x<='1';
    y<='1';
    z<='0';
    wait for 100 ns;
    x<='1';
    y<='1';
    z<='1';


    wait;
end process;
```

### TEST BENCH RESULTS:

 

3.)

Circuit Diagram:

 

## VHDL Implementation:

```

entity decoder24 is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          D : out STD_LOGIC_VECTOR (3
downto 0));
end decoder24;

architecture Behavioral of decoder24 is

begin

D(0) <= (not A) and (not B);
D(1) <= (not A) and B;
D(2) <= A and (not B);
D(3) <= A and B;

end Behavioral;

```

```

entity COMP24 is
    Port ( A : in  STD_LOGIC_VECTOR (1
downto 0);
          B : in  STD_LOGIC_VECTOR (1
downto 0);
          G : out  STD_LOGIC;
          E : out  STD_LOGIC;
          L : out  STD_LOGIC);
end COMP24;

architecture Behavioral of COMP24 is

COMPONENT decoder24
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          D : out  STD_LOGIC_VECTOR (3
downto 0));
end COMPONENT;


signal T : STD_LOGIC_VECTOR (7 downto 0);
begin

D1 : decoder24 port map(A(0),B(0),T(3
downto 0));
D2 : decoder24 port map(A(1),B(1),T(7
downto 4));

G <= T(6) or ((T(7) or T(4)) and T(2)) ;
L <= T(5) or ((T(7) or T(4)) and T(1)) ;
E <= (T(7) or T(4)) and (T(3) or T(0));
end Behavioral;

```


## RLT Schematic:

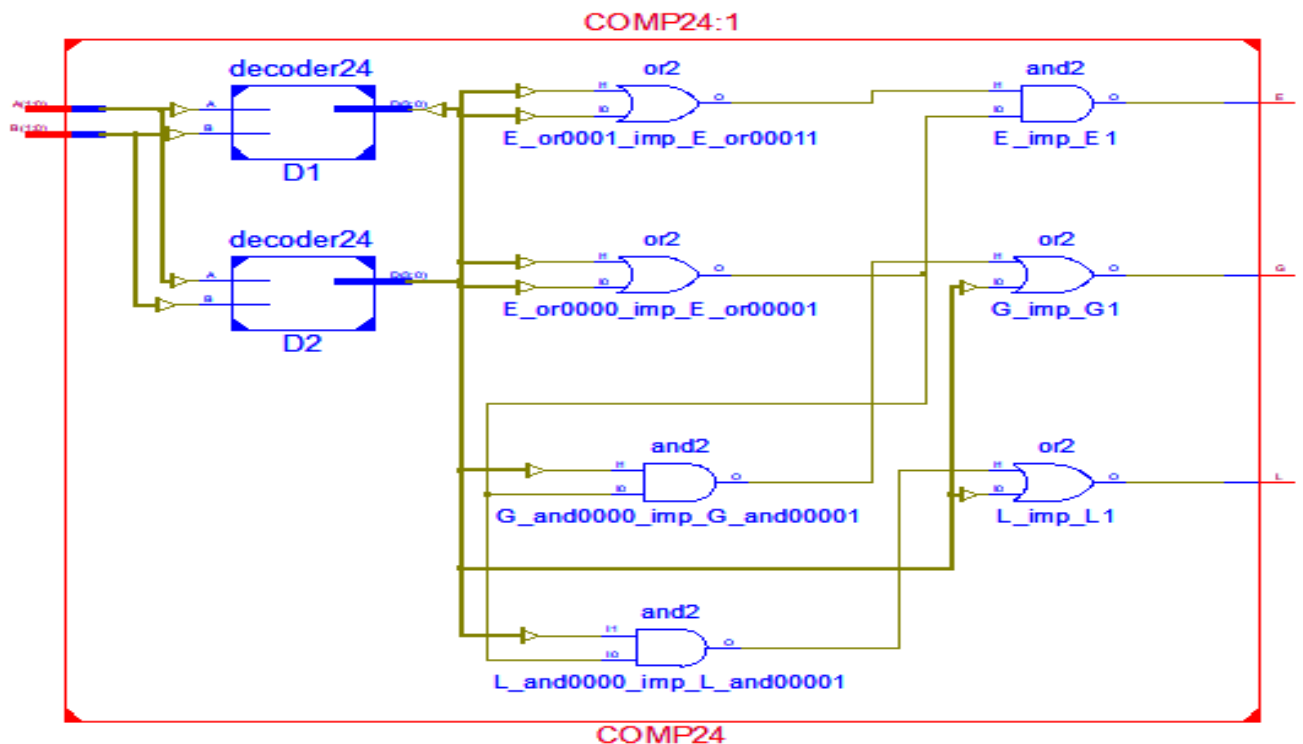

### TEST BENCH INPUT:

```
stim_proc: process
begin
    A <= "00";
    B <= "00";
    wait for 100 ns;
    A <= "00";
    B <= "10";
    wait for 100 ns;
    A <= "00";
    B <= "11";
    wait for 100 ns;
    A <= "01";
    B <= "00";
    wait for 100 ns;
    A <= "01";
    B <= "01";
    wait for 100 ns;
    A <= "10";
    B <= "01";
    wait for 100 ns;
    A <= "10";
    B <= "10";
    wait for 100 ns;
    A <= "10";
    B <= "11";
    wait for 100 ns;
    A <= "11";
    B <= "10";
    wait for 100 ns;
    A <= "11";
    B <= "11";
    wait;
end process;
```


### TEST BENCH RESULTS:

 



4.)

Circuit Diagram:

 

VHDL Implementation

```
entity ShiftAdder is
    Port ( A : in  STD_LOGIC_VECTOR (3 downto 0);
          S : out  STD_LOGIC_VECTOR (3 downto 0));
end ShiftAdder;

architecture Behavioral of ShiftAdder is

begin

    S(0)<= ((not A(3)) and (not A(2)) and A(0))or
    ((not A(3)) and A(2) and A(1) and (not A(0)))or
    (A(3) and (not A(2)) and (not A(1)) and (not A(0)));

    S(1)<= ((not A(3)) and (not A(2)) and A(1))or
    ((not A(3)) and A(1) and A(0))or
    (A(3) and (not A(2)) and (not A(1)) and (not A(0)));

    S(2)<= (A(3) and (not A(2)) and (not A(1)) and A(0))or
    ((not A(3)) and A(2) and (not A(1)) and (not A(0)));

    S(3)<= ((not A(3)) and A(2) and A(0))or
    ((not A(3)) and A(2) and A(1))or (A(3) and (not A(2)) and (not A(1)));

end Behavioral;
```

```
entity Converter is
    Port ( A : in  STD_LOGIC_VECTOR (5 downto 0);
          B : out  STD_LOGIC_VECTOR (6 downto 0));
end Converter;


architecture Behavioral of Converter is

component ShiftAdder
    Port ( A : in  STD_LOGIC_VECTOR (3 downto 0);
          S : out  STD_LOGIC_VECTOR (3 downto 0));
end component;

signal T : STD_LOGIC_VECTOR (9 downto 0);
signal K : STD_LOGIC_VECTOR (3 downto 0);
begin
    K(3)<= '0';
    K(2)<= A(5);
    K(1)<= A(4);
    K(0)<= A(3);
    B(6)<= T(9);
    T(5)<= A(2);
    B(5)<= T(4);
    T(0)<= A(1);
    SA1 : ShiftAdder port map (K(3 downto 0),T(9 downto 6));
    SA2 : ShiftAdder port map (T(8 downto 5),T(4 downto 1));
    SA3 : ShiftAdder port map (T(3 downto 0),B(4 downto 1));
    B(0) <= A(0);

end Behavioral;
```

### RLT Schematic:

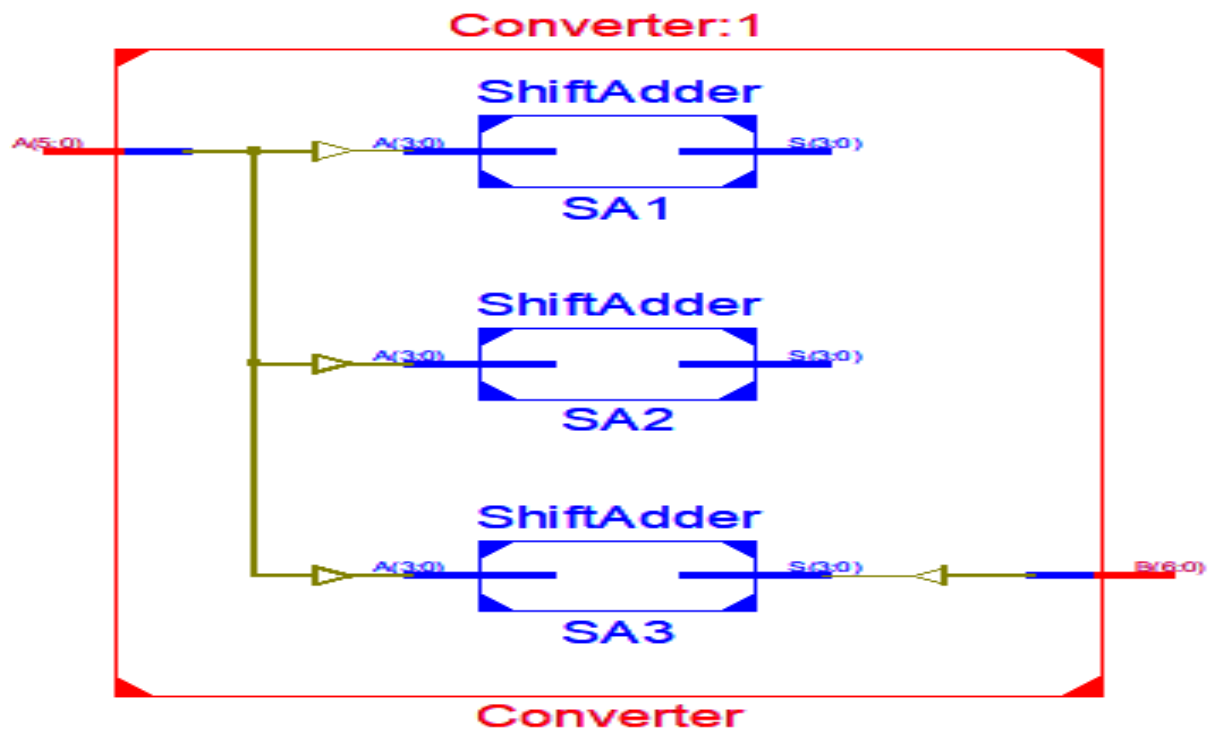

### TEST BENCH INPUT:

```
stim_proc: process
begin
    A <= "101010";
    wait for 100 ns;
    A <= "010101";
    wait for 100 ns;
    A <= "111111";
    wait for 100 ns;
    A <= "111110";
    wait for 100 ns;
    A <= "010110";
    wait for 100 ns;
    A <= "010001";
    wait for 100 ns;
    A <= "011011";
    wait for 100 ns;
    A <= "101101";

    wait;
end process;
```

TEST BENCH RESULTS:

