



Egemen Can AYDUĞAN - 21728036

1-A) S-R Latch Circuit Diagram



VHDL Implementation:


```
entity SRLatch is
    Port ( S : in  STD_LOGIC;
          R : in  STD_LOGIC;
          Q : out STD_LOGIC;
          Qn : out STD_LOGIC);
end SRLatch;

architecture Behavioral of SRLatch is

    signal T : STD_LOGIC_VECTOR(1 downto 0);

begin
    Q <= S nand T(1);
    Qn <= R nand T(0);
    T(0) <= S nand T(1);
    T(1) <= R nand T(0);
end Behavioral;
```

RTL Schematic:

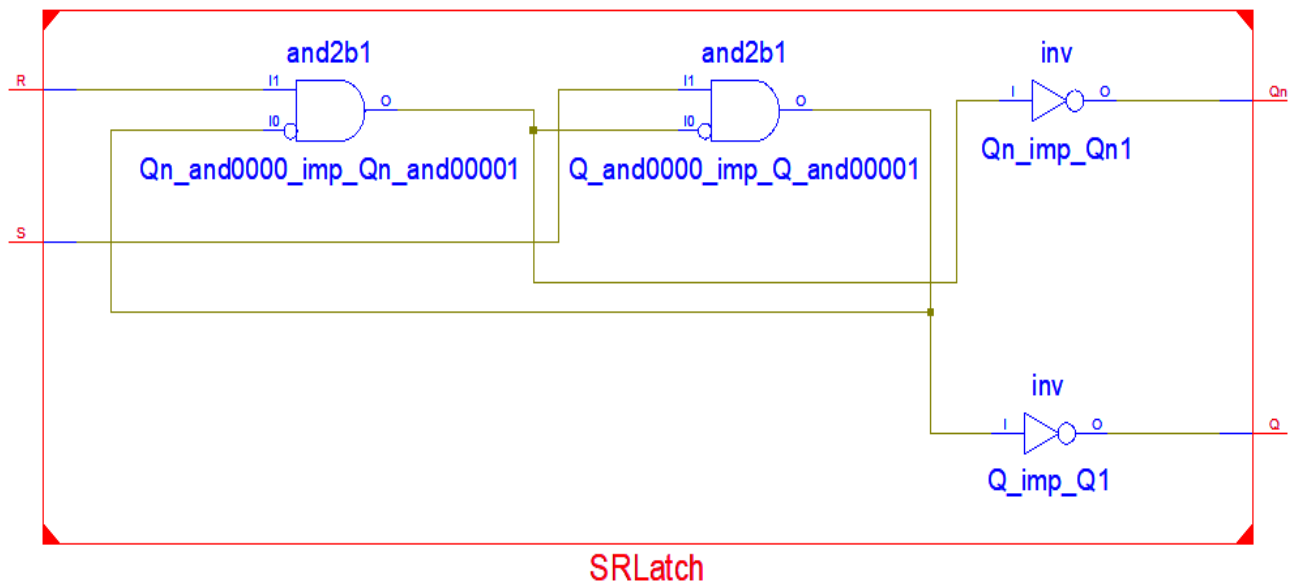

1-B) D Latch

Circuit Diagram



VHDL Implementation:

```
entity DLatch is
    Port ( D : in  STD_LOGIC;
          En : in  STD_LOGIC;
          Q : out  STD_LOGIC;
          Qn : out  STD_LOGIC);
end DLatch;


architecture Behavioral of DLatch is

    component SRLatch
        Port ( S : in  STD_LOGIC;
              R : in  STD_LOGIC;
              Q : out  STD_LOGIC;
              Qn : out  STD_LOGIC);
    end component;

    signal K : STD_LOGIC_VECTOR(1 downto 0);


begin
    K(0) <= D nand En;
    K(1) <= (not D) nand En;
    C : SRLatch port map (K(0),K(1),Q,Qn);
end Behavioral;
```

RTL Schematic:

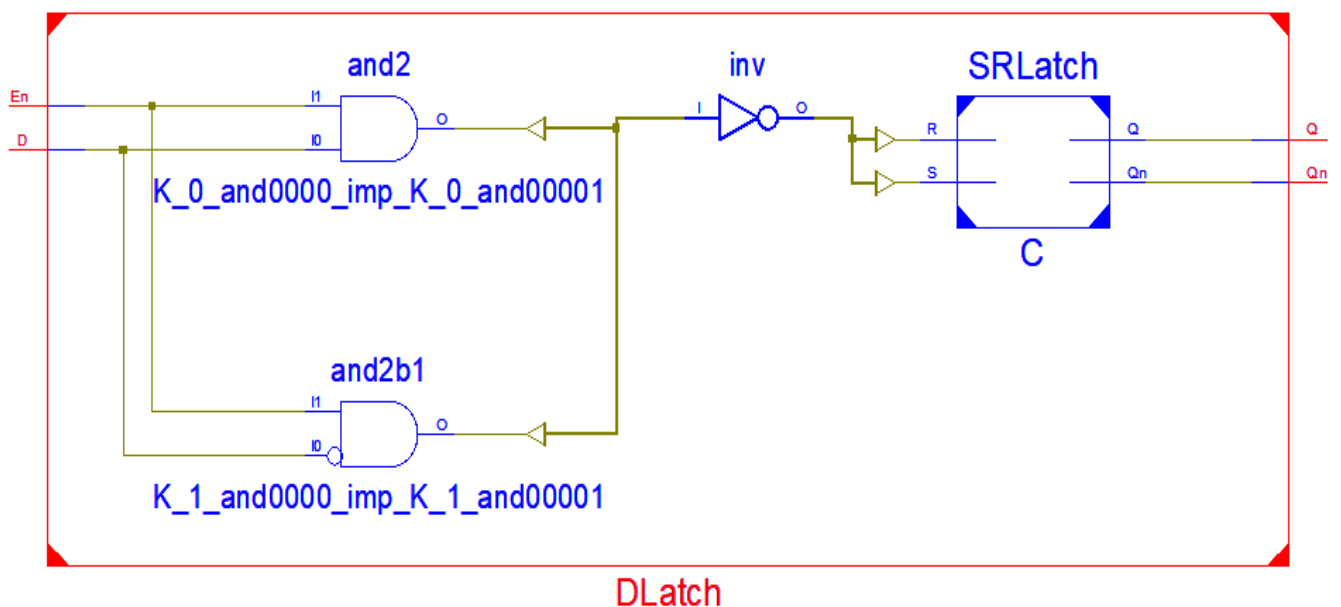

1-C) Positive Edge D Flip-Flop

Circuit Diagram

 

VHDL Implementation:

```
entity DFlipFlop is
    Port ( D : in  STD_LOGIC;
          Clk : in  STD_LOGIC;
          Q : out  STD_LOGIC;
          Qn : out  STD_LOGIC);
end DFlipFlop;


architecture Behavioral of DFlipFlop is

    component DLatch
        Port ( D : in  STD_LOGIC;
              En : in  STD_LOGIC;
              Q : out  STD_LOGIC;
              Qn : out  STD_LOGIC);
    end component;

    signal T : STD_LOGIC_VECTOR(1 downto 0);


begin
    C1 : DLatch port map(D,Clk,T(0),T(1));
    C2 : DLatch port map(T(0),(not Clk),Q,Qn);
end Behavioral;
```

RTL Schematic:

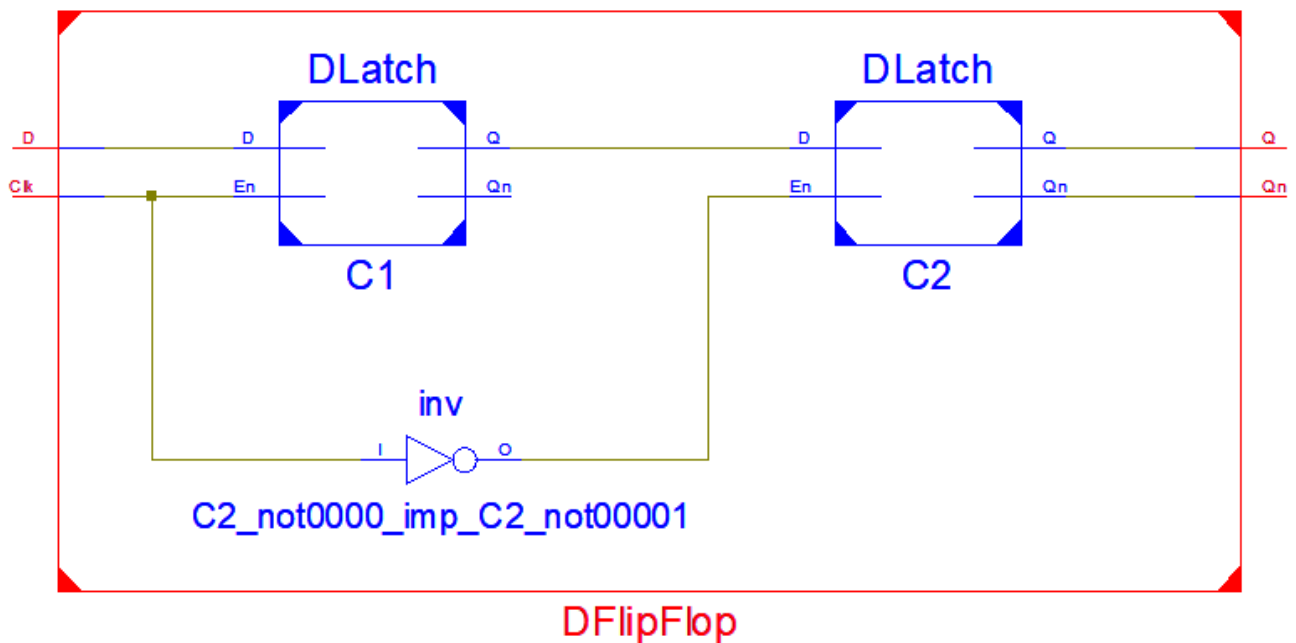

1-D) Negative Edge T Flip-Flop

Circuit Diagram

 


VHDL Implementation:

```
entity NegTFlipFlop is
    Port ( T : in  STD_LOGIC;
          Reset : in  STD_LOGIC;
          Clk : in  STD_LOGIC;
          Q : out  STD_LOGIC;
          Qn : out  STD_LOGIC);
end NegTFlipFlop;
architecture Behavioral of NegTFlipFlop is


    component JKFlipFlop
        Port ( J : in  STD_LOGIC;
              K : in  STD_LOGIC;
              Reset : in  STD_LOGIC;
              Clk : in  STD_LOGIC;
              Q : out  STD_LOGIC;
              Qn : out  STD_LOGIC);
    end component;

begin
    C : JKFlipFlop port map (T,T,Reset,(not Clk),Q,Qn);
end Behavioral;
```

RTL Schematic:

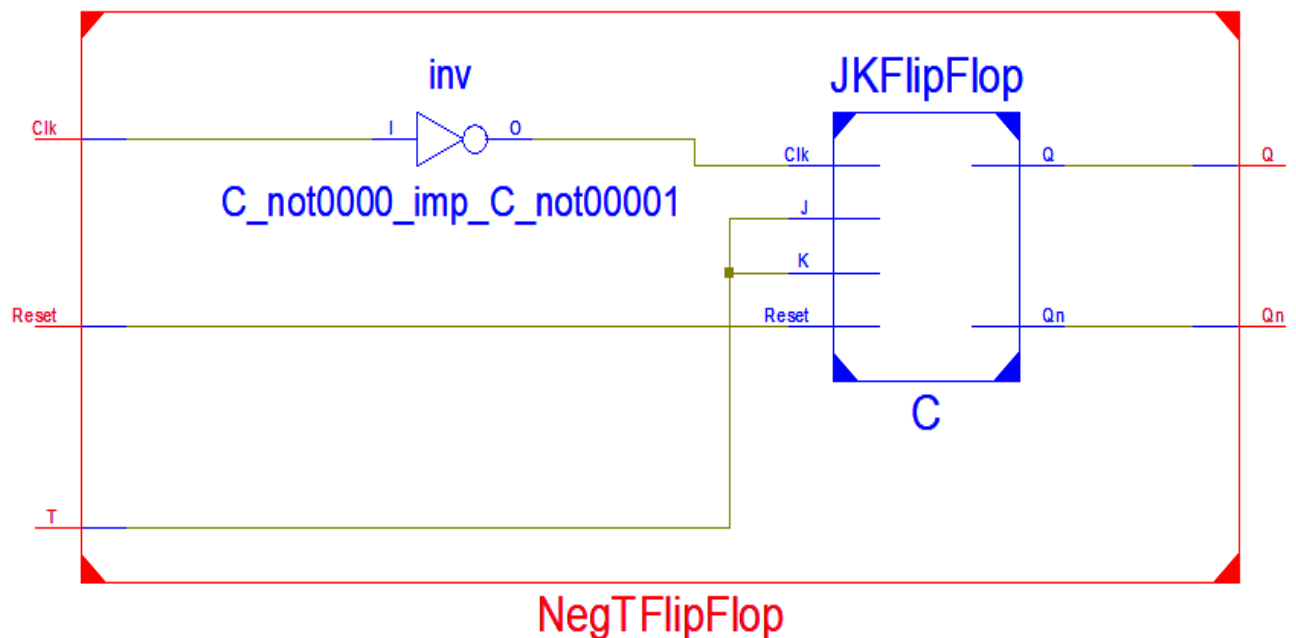

2) Circuit Diagram

 

VHDL Implementation:

```

entity SequenceDetector is
    Port ( X : in  STD_LOGIC;
          Reset : in  STD_LOGIC;
          Clk : in  STD_LOGIC;
          Y : out  STD_LOGIC);
end SequenceDetector;

architecture Behavioral of SequenceDetector is

    component JKFlipFlop
        Port ( J : in  STD_LOGIC;
              K : in  STD_LOGIC;
              Reset : in  STD_LOGIC;
              Clk : in  STD_LOGIC;
              Q : out  STD_LOGIC;
              Qn : out  STD_LOGIC);
    end component;

    signal JA,JB,JC,KA,KB,KC : STD_LOGIC;
    signal A,B,C : STD_LOGIC;
    begin

        JA <= B and C and x;
        KA <= '1';
        JB <= (A and (not x)) or (C and (not x));
        KB <= x or C;
        JC <= x or B;
        KC <= (not x) or B;


        FF1 : JKFlipFlop port map(JA,KA,Reset,Clk,A);
        FF2 : JKFlipFlop port map(JB,KB,Reset,Clk,B);
        FF3 : JKFlipFlop port map(JC,KC,Reset,Clk,C);

        Y <= A;

    end Behavioral;

```

RTL Schematic:

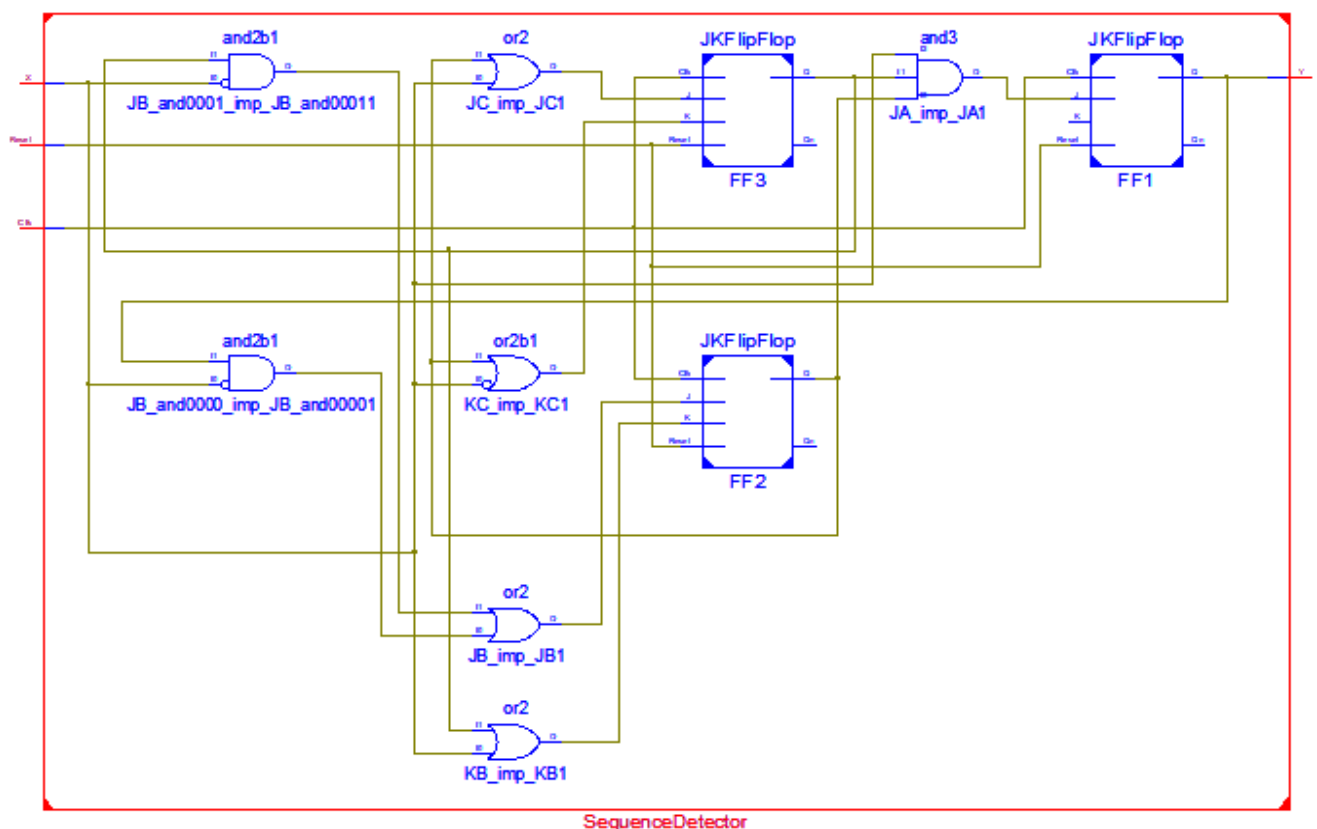


Test Bench Input

```
constant Clk_period : time := 100 ns;


Clk_process :process
begin
    Clk <= '1';
    wait for Clk_period/2;
    Clk <= '0';
    wait for Clk_period/2;
end process;

stim_proc: process
begin
    -- hold reset state for 100 ns.
    Reset <= '1';
    wait for 100 ns;
    x <= '1';
    Reset <= '0';
    wait for 100 ns;
    x <= '0';
    wait for 100 ns;
    x <= '0';
    wait for 100 ns;
    x <= '1';
    wait for 100 ns;
    x <= '0';
    wait for 100 ns;
    x <= '0';
    wait for 100 ns;
    x <= '1';
    wait;
end process;
```

Test Bench Result

 

3) Circuit Diagram

 

VHDL Implementation:

```
entity ODDParity is
    Port ( D : in  STD_LOGIC_VECTOR (11 downto 0);
          Pin : in  STD_LOGIC;
          Reset : in  STD_LOGIC;
          Clock : in  STD_LOGIC;
          Pout : out  STD_LOGIC;
          Pche : out  STD_LOGIC);
end ODDParity;


architecture Behavioral of ODDParity is

    component TFF
        Port ( T : in  STD_LOGIC;
              Reset : in  STD_LOGIC;
              Clock : in  STD_LOGIC;
              Q : out  STD_LOGIC;
              Qn : out  STD_LOGIC);
    end component;

    signal T1,T2,T3 : STD_LOGIC;
begin
    T1 <= D(0) xor D(1) xor D(2) xor D(3) xor
    D(4) xor D(5) xor D(6) xor D(7) xor
    D(8) xor D(9) xor D(10) xor D(11) ;

    FF : TFF port map(T1,Reset,Clock,T2,T3);
    Pout <= T2;
    Pche <= Pin xnor T2;
end Behavioral;
```


RTL Schematic:

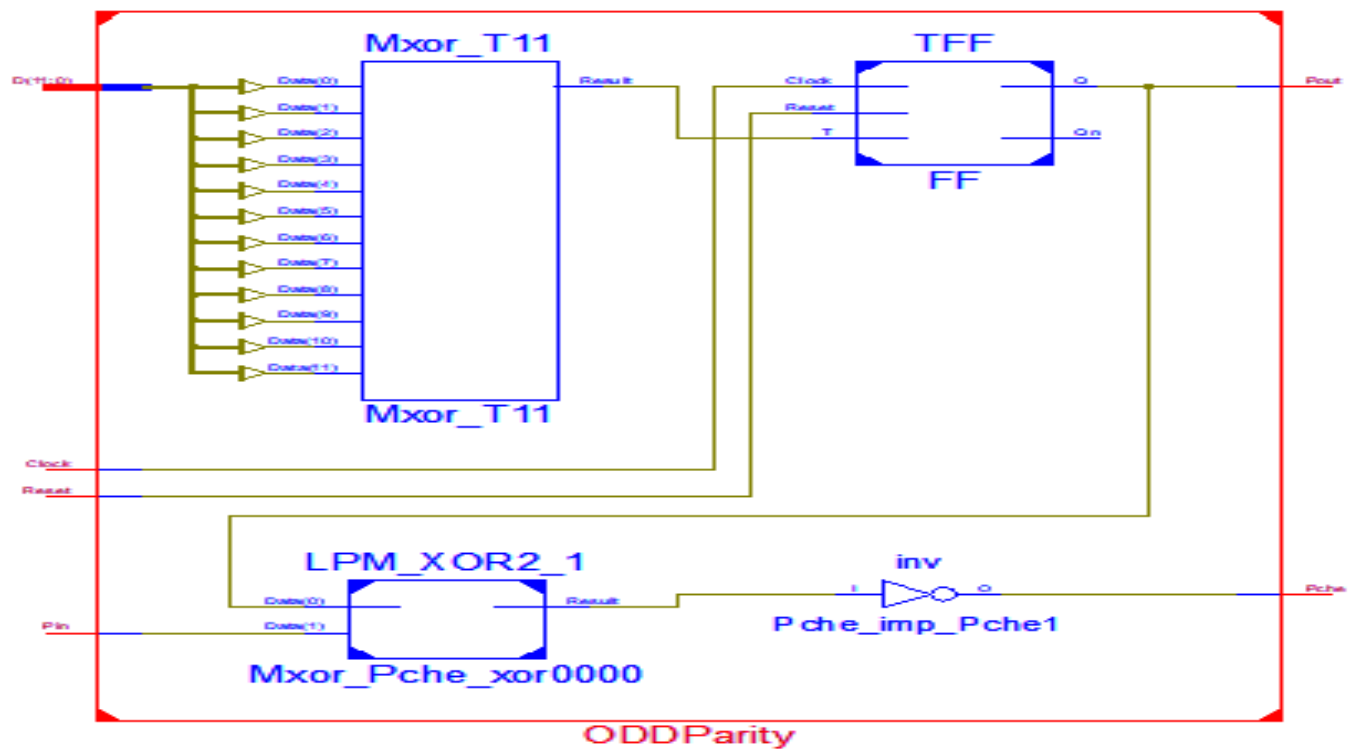

Test Bench Input

```
constant Clock_period : time := 100 ns;


Clock_process :process
begin
    Clock <= '1';
    wait for Clock_period/2;
    Clock <= '0';
    wait for Clock_period/2;
end process;

begin


    Reset <= '1';
    wait for 100 ns;
    D <= "101101010110";
    Pin <= '1';
    Reset <= '0';
    wait for 100 ns;
    D <= "111100101101";
    Pin <= '1';
    wait for 100 ns;
    D <= "000000001010";
    Pin <= '0';
    wait for 100 ns;
    D <= "111111111111";
    Pin <= '0';

    wait;
end process;
```

Test Bench Result

 

4) Circuit Diagram

 


VHDL Implementation:

```
entity JFF is
    Port ( J : in  STD_LOGIC;
          K : in  STD_LOGIC;
          Reset : in  STD_LOGIC;
          Clock : in  STD_LOGIC;
          Q : out  STD_LOGIC;
          Qn : out  STD_LOGIC);
end JFF;

architecture Behavioral of JFF is
    component DFF
        Port ( D : in  STD_LOGIC;
              Reset : in  STD_LOGIC;
              Clock : in  STD_LOGIC;
              Q : out  STD_LOGIC;
              Qn : out  STD_LOGIC);
    end component;
    signal T1,T2,T3,T4,T5 : STD_LOGIC;
begin
    T1 <= J and T5;
    T2 <= (not K) and T4;
    T3 <= T1 or T2;
    FF : DFF port map (T3,Reset,Clock,T4,T5);
    Q <= T4;
    Qn <= T5;
end Behavioral;
```

RTL Schematic:

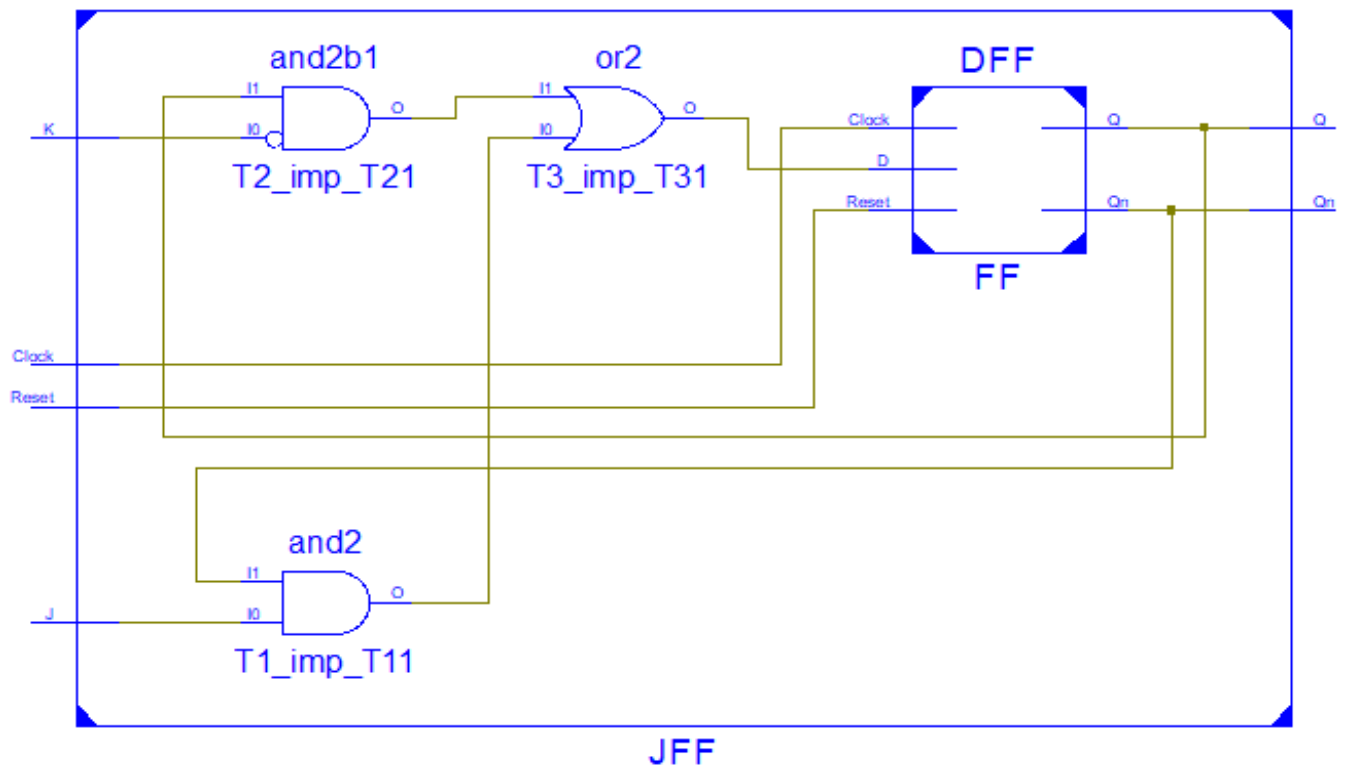

Test Bench Input

```

constant Clock_period : time := 100 ns;

-- Clock process definitions
Clock_process :process
begin
    Clock <= '0';
    wait for Clock_period/2;
    Clock <= '1';
    wait for Clock_period/2;
end process;

stim_proc: process
begin
    Reset <= '1';
    wait for 100 ns;
    J <= '0';
    K <= '0';
    Reset <= '0';
    wait for 100 ns;
    J <= '0';
    K <= '1';
    wait for 100 ns;
    J <= '1';
    K <= '0';
    wait for 100 ns;
    J <= '1';
    K <= '1';
    wait;
end process;

```

Test Bench Result

